



# EE 101: Basic Electronics

## Bipolar Junction Transistor


Nagarjuna Nallam

Department of EEE, IIT Guwahati, India

# Diode $\rightarrow$ Transistor

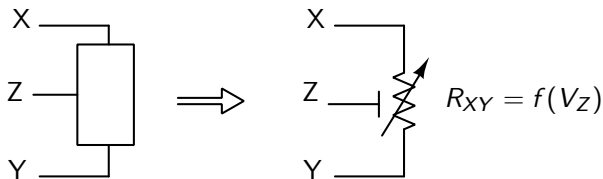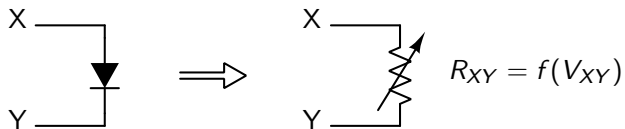

# Transistor another description


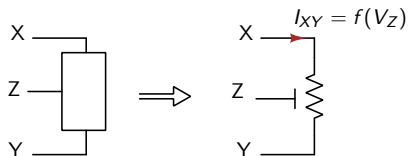


$I_{XY} = f(V_Z) \Rightarrow$  Transconductance device

$$\text{Small-signal transconductance} = \frac{\partial I_{XY}}{\partial V_Z} = f'(V_Z)$$

Recap: Small-signal gain = slope of the DC transfer curve at the given bias
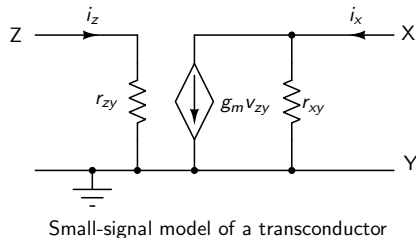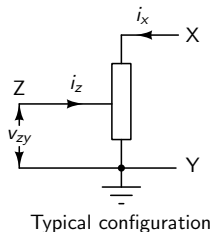
# Typical configuration and small-signal model





$$g_m = \frac{\partial I_X}{\partial V_{ZY}}$$


$$r_{zy} = \frac{\partial V_{ZY}}{\partial I_Z}$$

$$r_{xy} = \frac{\partial V_{XY}}{\partial I_X}$$


# Bipolar Junction Transistor

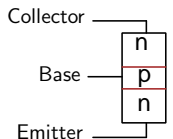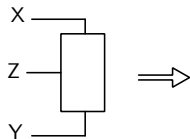


npn transistor

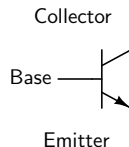

Circuit symbol of npn BJT

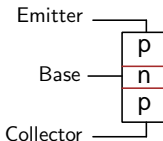


pnp transistor

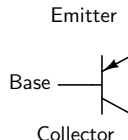


Circuit symbol of pnp BJT

# Two Junctions - Four Possibilities

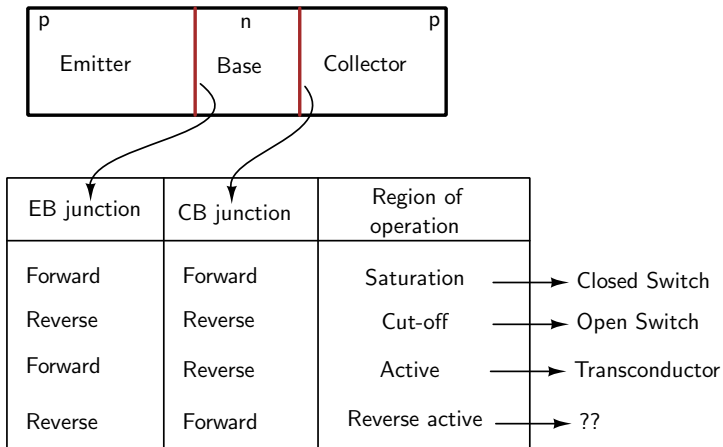

# Active Region of Operation

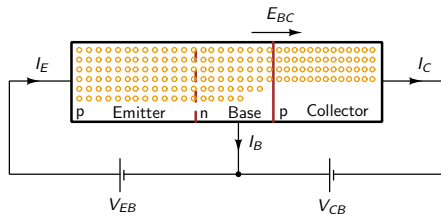

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E \quad 0 < \alpha < 1$$


$$I_C = \beta I_B \quad \beta \gg 1$$

$$I_C \approx I_0 e^{V_{EB}/V_T}$$


$\alpha$  is known as the common-base current gain

$\beta$  is known as the common-emitter current gain

# Characteristics of pnp Transistor

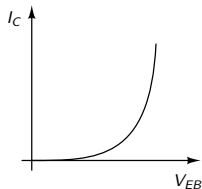


$$I_C = I_0 e^{V_{EB}/V_T}$$

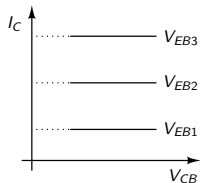


$I_C$  is independent of  $V_{CB}$



# Small-signal model of a BJT

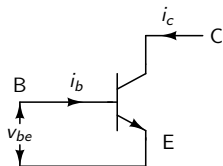

Typical configuration

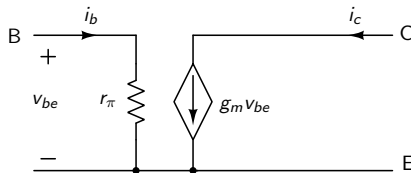


Small-signal model of a transconductor

$$g_m = \frac{\partial I_C}{\partial V_{BE}} = \frac{I_C}{V_T}$$

$$r_\pi = \frac{\partial V_{BE}}{\partial I_B} = \frac{V_T}{I_B}$$

# Early effect and output impedance

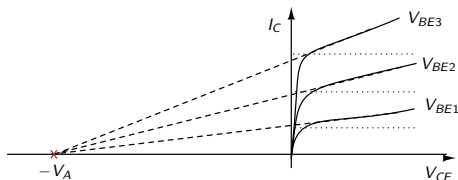

$I_C$  depends on  $V_{CB}$


Modified current equation:  $I_C \approx I_0 e^{V_{BE}/V_T} (1 + \frac{V_A}{V_{CE}})$

$$\text{Output resistance } r_0 = \frac{\partial V_{CE}}{\partial I_C} \approx \frac{V_A + V_{CE}}{I_C}$$


$V_A$  is called the Early voltage.

Alternatively,  $r_0 \approx \frac{V_A}{I'_C}$ ;  $I'_C$  is the collector current without Early effect.

# Small-signal model of a BJT

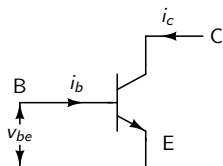

Typical configuration

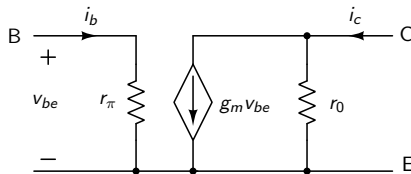

Small-signal model of a transconductor

$$g_m = \frac{\partial I_C}{\partial V_{BE}} = \frac{I_C}{V_T}$$

$$r_\pi = \frac{\partial V_{BE}}{\partial I_B} = \frac{V_T}{I_B}$$

$$r_0 = \frac{\partial V_{CE}}{\partial I_C} \approx \frac{V_A}{I_C}$$

# Summary

- ▶ Transistor
- ▶ Generic small-signal model of a transconductor
- ▶ BJT
- ▶ Operation of a BJT in active mode/region
- ▶ I-V relations
- ▶ Small-signal model of a BJT

# Reference Book

[1] A. Sedra and K. C. Smith, "Microelectronic Circuits," 6th Ed., Oxford university press, 2011.