


EE 101: Basic Electronics

Diode Basics


Nagarjuna Nallam

Department of EEE, IIT Guwahati, India

Linear Elements

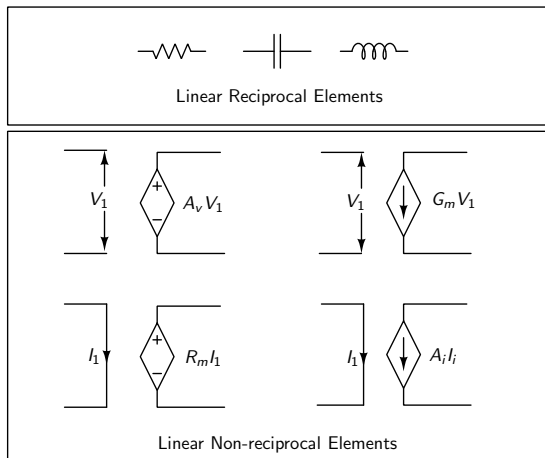

A Two Terminal Non-Linear Element

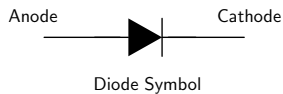


Non-linear + Non-Reciprocal

An Ideal Diode


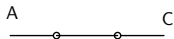
$$R_{AC} = \begin{cases} 0 & \text{for } V_{AC} > 0 \\ \infty & \text{for } V_{AC} < 0 \end{cases}$$



Equivalent Circuit

for $V_{AC} > 0$

Diode is forward biased




Equivalent Circuit





for $V_{AC} < 0$

Diode is reverse biased



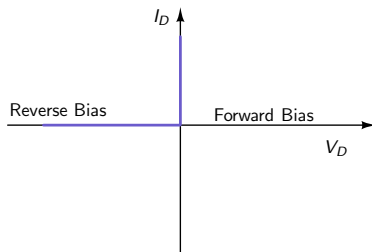
$I - V$ Characteristics of an Ideal Diode








A Diode Circuit

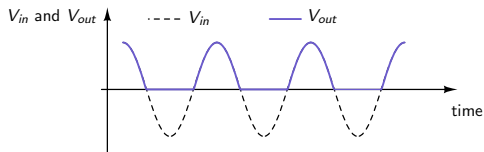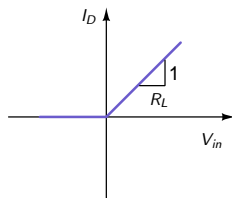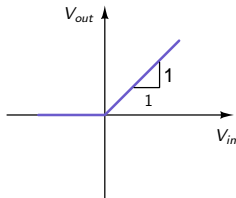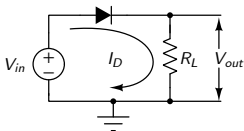



A Diode Circuit

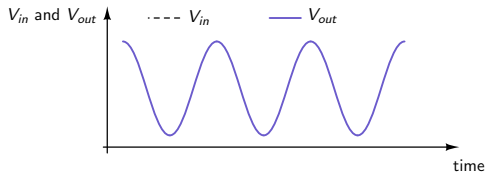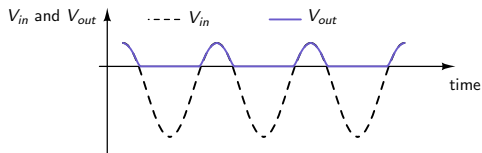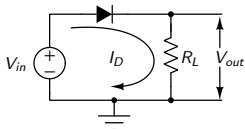



Draw the Transfer Characteristics

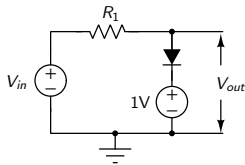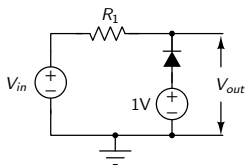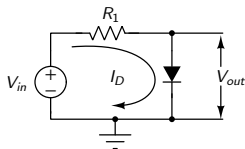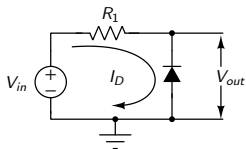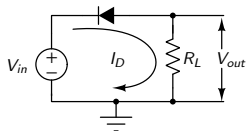


A Real Diode

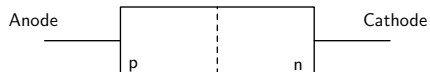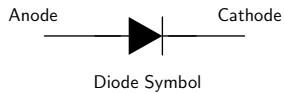

A PN Junction Diode

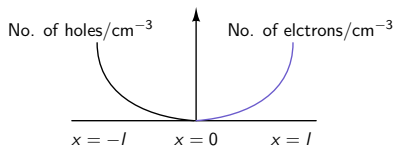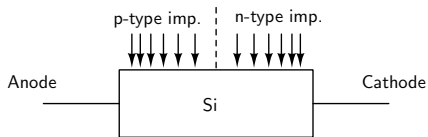


Diffusion Current in a PN Junction Diode

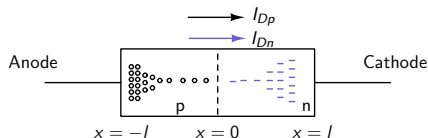


$$\text{Diffusion Current } I_D = I_{Dp} + I_{Dn}$$

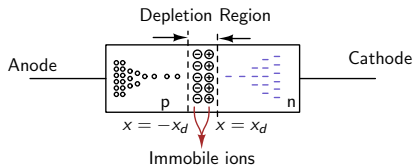Quick Recap: Diffusion current \propto Carrier Gradient



Drift Current in a PN Junction Diode

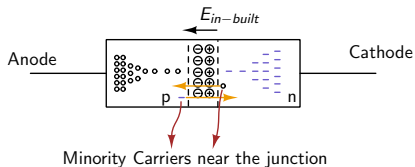


Quick Recap: Drift Current $\propto E$

Direction of drift current due to $E_{in-built}$ is $n \rightarrow p$

At equilibrium: Diffusion current = Drift current

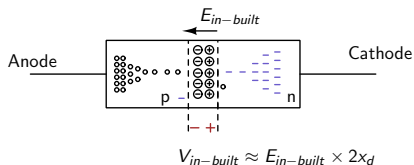Built-in potential in a PN Junction Diode



$$V_{in-built} = V_T \ln \left(\frac{N_A N_D}{n_i^2} \right),$$

Where $V_T = \frac{kT}{q}$ is the thermal voltage,


N_A is the acceptor atoms concentration on p-side,

N_D is the donor atoms concentration on n-side,

n_i is the intrinsic carrier concentration.

$$\text{In Si PN junction diodes, } V_{in-built} \approx 0.7V$$

PN Junction Diode in Reverse Bias

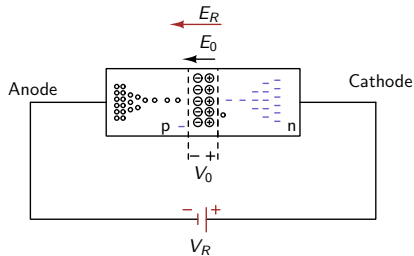


In reverse bias, drift current > diffusion current

↓
due to minority carriers

↓
small current from $n \rightarrow p$

PN Junction Diode in Forward Bias

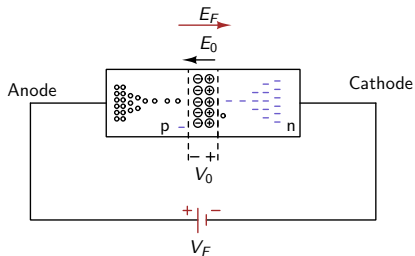


In Forward bias, diffusion current > drift current

↓
due to majority carriers

↓
small current from $p \rightarrow n$ for $V_F < V_0$

large current from $p \rightarrow n$ for $V_F \geq V_0$

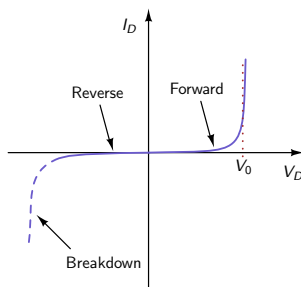I-V Characteristics of a PN Junction Diode




$$I_D = \begin{cases} I_s \left(e^{\left(\frac{V_D}{\eta V_T} \right)} - 1 \right) & \text{for } V_D > 0 \\ -I_s & \text{for } V_D < 0 \end{cases}$$


I_s is called saturation current.

η is a constant and has a value between 1 to 2.


Piecewise Linear Models

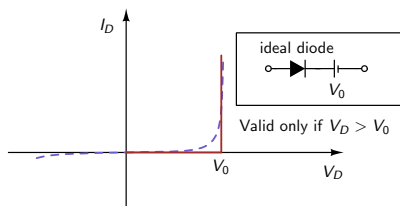

— Piecewise linear models

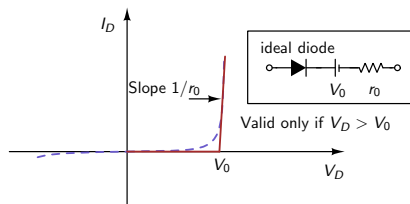

Draw the Transfer Characteristics

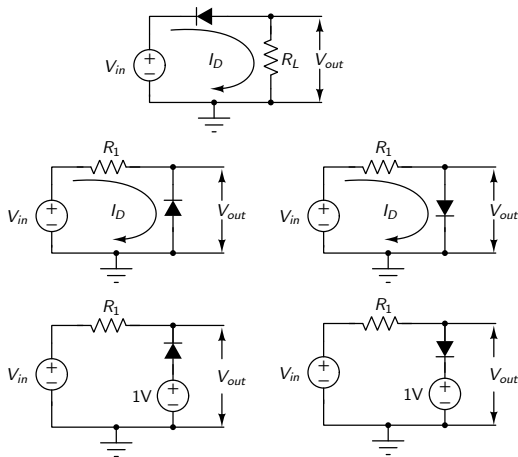

Assume Si based PN-junction diodes.

Summary

- ▶ Nonlinear, non-reciprocal element
- ▶ Ideal diode characteristics
- ▶ Review of semiconductor physics (not in slides)
- ▶ Operation of a PN junction diode
- ▶ I-V characteristics of a PN junction diode
- ▶ Piecewise linear models of a diode

Reference Book

[1] A. Sedra and K. C. Smith, "Microelectronic Circuits," 6th Ed., Oxford university press, 2011.