



Department of Electronics & Electrical Engineering





Lecture 5

The Forced Solution

By

Dr. Praveen Kumar

Professor

Department of Electronics & Electrical Engineering





The response to sinusoidal source

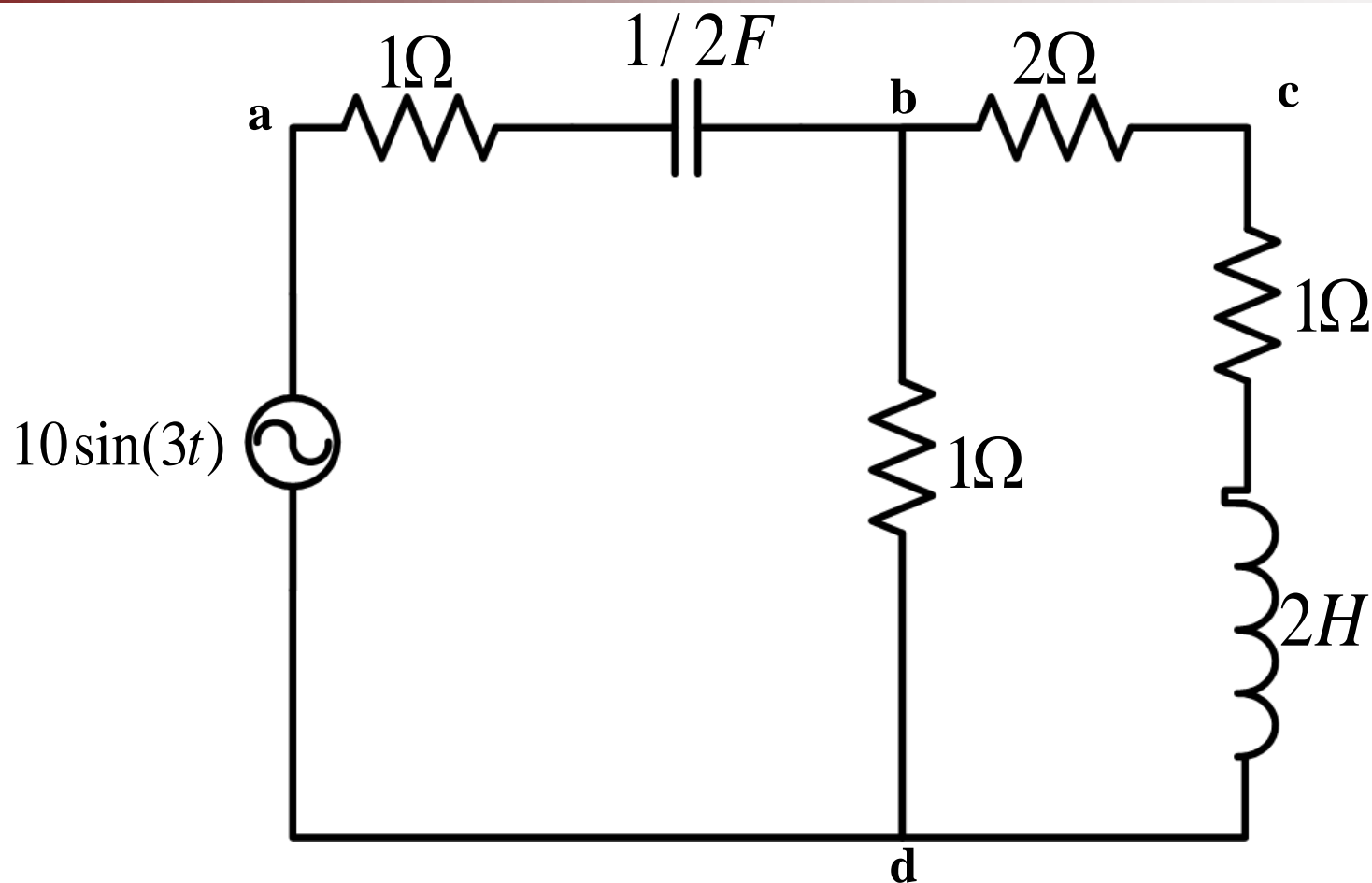


Figure 1: Network with sinusoidal excitation



The response to sinusoidal source

- In Fig.1, the excitation is

$$e_1(t) = 10\sin(3t) \quad (1)$$

- The equilibrium equation is found from the relationship

$$i_f(t) = \frac{1}{Z_{ad}} e_1(t) = \left(\frac{2p^2 + 4p}{4p^2 + 11p + 8} \right) 10\sin(3t) \quad (2)$$

- Rearranging the terms of eq.2 gives

$$(4p^2 + 11p + 8)i_f(t) = (2p^2 + 4p)10\sin(3t) \quad (3)$$

- The right hand side of eq.3 is simplified as

$$(2p^2 + 4P)10\sin(3t) = -180\sin(3t) + 120\cos(3t) \quad (4)$$

- The eq.4 clearly indicates that the assumed form of the forced solution must contain both a *sine* and a *cosine* component in order to have left hand side equal to the right hand side.



The response to sinusoidal source

- The assumed solution is

$$i_f(t) = A \sin(3t) + B \cos(3t) \quad (5)$$

$$p i_f(t) = \frac{d i_f(t)}{dt} = 3A \cos(3t) - 3B \sin(3t) \quad (6)$$

$$p^2 i_f(t) = -9A \sin(3t) - 9B \cos(3t) \quad (7)$$

- Using eq.5 to 7 to substitutes the values of $i_f(t)$, $p i_f(t)$ and $p^2 i_f(t)$ into eq.4 gives

$$(-28A - 33B) \sin(3t) + (33A - 28B) \cos(3t) = -180 \sin(3t) + 120 \cos(3t) \quad (8)$$

- Equating the coefficients of $\sin(3t)$ and $\cos(3t)$ in eq.22 gives

$$28A + 33B = 180 \quad (9)$$

$$33A - 28B = 120 \quad (10)$$

$$\Rightarrow A = 4.8 \text{ and } B = 1.38$$

- The complete forced solution is

$$i_f(t) = 4.8 \sin(3t) + 1.38 \cos(3t) \quad (11)$$





The response to Polynomial Sources

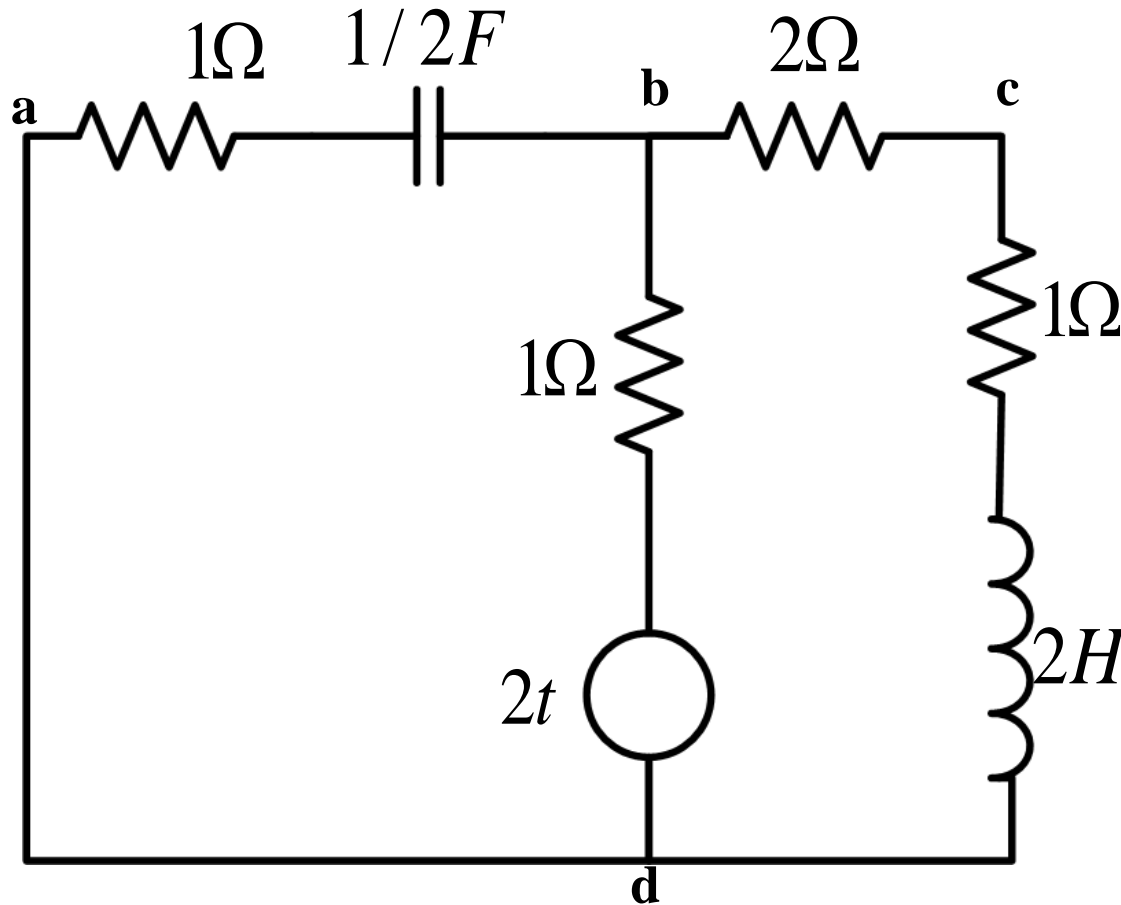


Fig.2: Network with sinusoidal excitation



The response to Polynomial Sources

- The excitation function in the Fig.2 is

$$f(t) = 2t \quad (12)$$

- The function in eq.12 varies linearly with time and has a slope of 2. Because of its sloping graphical representation, eq.12 is also referred to as *ramp function*.

- The current $i_f(t)$ is given by

$$i_f(t) = \frac{1}{Z} e(t) = \frac{2p^2 + 4p + 2}{4p^2 + 11p + 8} (2t) \quad (13)$$

- Rearranging the eq.13 gives

$$(4p^2 + 11p + 8)i_f(t) = (2p^2 + 4p + 2)(2t) \quad (14)$$

- Simplifying eq.14 gives

$$(4p^2 + 11p + 8)i_f(t) = 8 + 4t \quad (15)$$





The response to Polynomial Sources

- The forced response can be written as the sum of a constant term plus a ramp. Hence

$$i_f(t) = A + Bt \quad (16)$$

- Substituting $i_f(t)$ from eq.16 into eq.15 gives

$$11B + 8A + 8Bt = 8 + 4t \quad (17)$$

- Equating the like coefficients and solving for the unknown quantities gives

$$A = \frac{5}{16}, B = \frac{1}{2} \quad (18)$$

- The complete expression for the forced solution becomes

$$i_f(t) = \frac{5}{16} + \frac{1}{2}t \quad (19)$$



The Natural Response (Transient Solution)

- The forced solution is the solution that is found to exist when the circuit has settled down in its response to the disturbing effect of an applied source function. **This forced solution is also known as *steady state solution*.**
- The forced or the steady state solution always satisfies the defining differential equation but in general it *is not a valid a solution over the entire time domain*.
- To illustrate the point consider the circuit shown in Fig.3. In this network it is desired to find the complete solution for the voltage v appearing across the resistor for all time t after the switch is closed.
- The equation that relates v to the source voltage E is

$$\frac{v}{E} = \frac{R}{R + pL} = \frac{1}{1 + p\left(\frac{L}{R}\right)} \quad (20)$$

$$\Rightarrow \frac{L}{R} \frac{dv}{dt} + v = E \quad (21)$$





The Natural Response (Transient Solution)

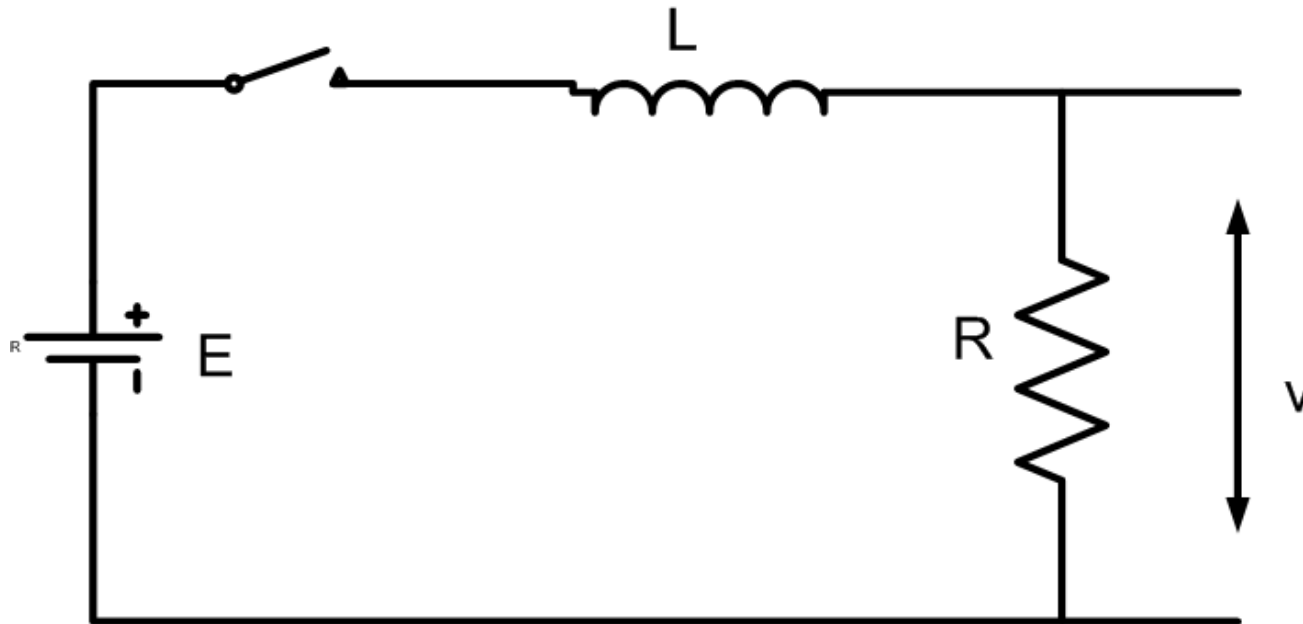



Fig.3: An R-L circuit



The Natural Response (Transient Solution)

- The forced solution of eq.21 is

$$v_f = E \quad (22)$$

- The solution in eq.22 satisfies eq.21, however this solution does not qualify as a solution of the governing differential equation in the period immediately following the closing of the switch at time $t = 0^+$
- At time $t = 0^+$ the current is zero because of the presence of the inductor. Hence v , which is iR , is also zero. Hence, the solution in eq.22 cannot be taken to be a complete description.
- In essence, then, there arises, in this time period, $t = 0^+$, immediately following the application of the source function, a need to add a **complementary function** to the forced solution.
- This complementary function will disappear as steady state is reached. It is the purpose of the **complementary function** to provide a smooth transition from the initial state of the response in the presence of **energy storing** elements to the final state. 



The Natural Response (Transient Solution)

- In Fig.3, the complementary function (natural response) is obtained by solving the equation

$$\frac{L}{R} \frac{dv}{dt} + v = 0 \quad (23)$$

- The solution to the eq.23 should satisfy that function, v and its derivative, dv/dt , must be of the same form to make the left hand side equal to the right hand side.
- The plausible solution for eq.23 is

$$v = Ke^{st} \quad (24)$$

- Substituting v from eq.24 into eq.23 gives

$$\left(\frac{L}{R} s + 1 \right) Ke^{st} = 0 \quad (25)$$

$$\Rightarrow s = -\frac{R}{L} \quad (26)$$





The Natural Response (Transient Solution)

- Hence, the complementary solution becomes

$$v = Ke^{-(R/L)t} \quad (27)$$

- The complete solution of the original governing differential equation (eq.23) is

$$v = E + Ke^{-(R/L)t} \quad (28)$$

- The quantity K is found from the initial condition which requires that v to be zero at $t=0^+$

$$0 = E + K \Rightarrow K = -E \quad (29)$$

- Hence, the complete solution is

$$v = E(1 - e^{-(R/L)t}) \quad (30)$$

- A graph of eq.30 is shown in Fig.4. The rapidity with which this transition takes place is entirely dependent upon the value s . In eq.26 when R is large (or L is small) the transition occurs quickly because the transient term dies out in little time.





The Natural Response (Transient Solution)

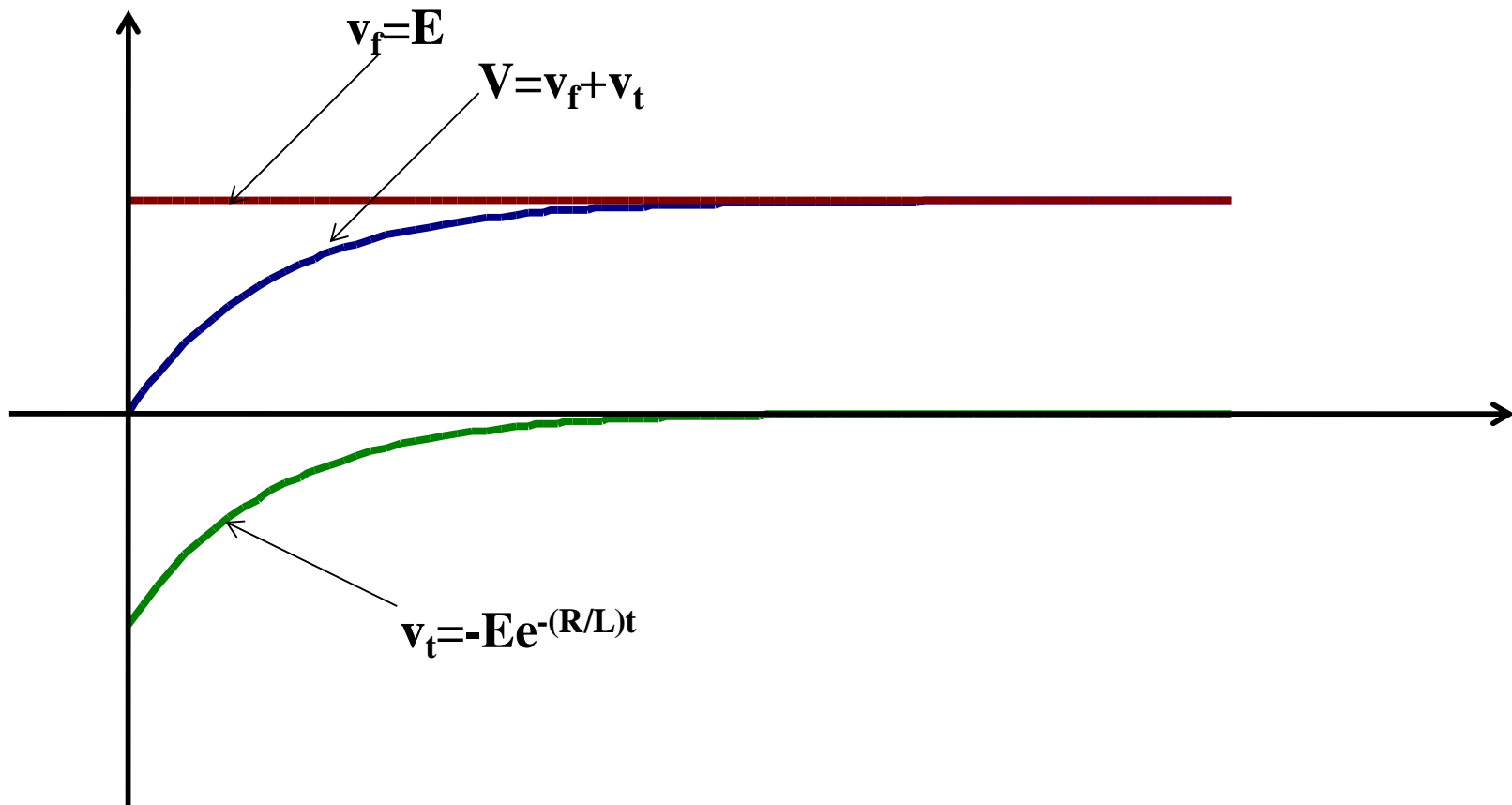


Fig.4: Complete solution of voltage across the resistor in network 3



Example 1

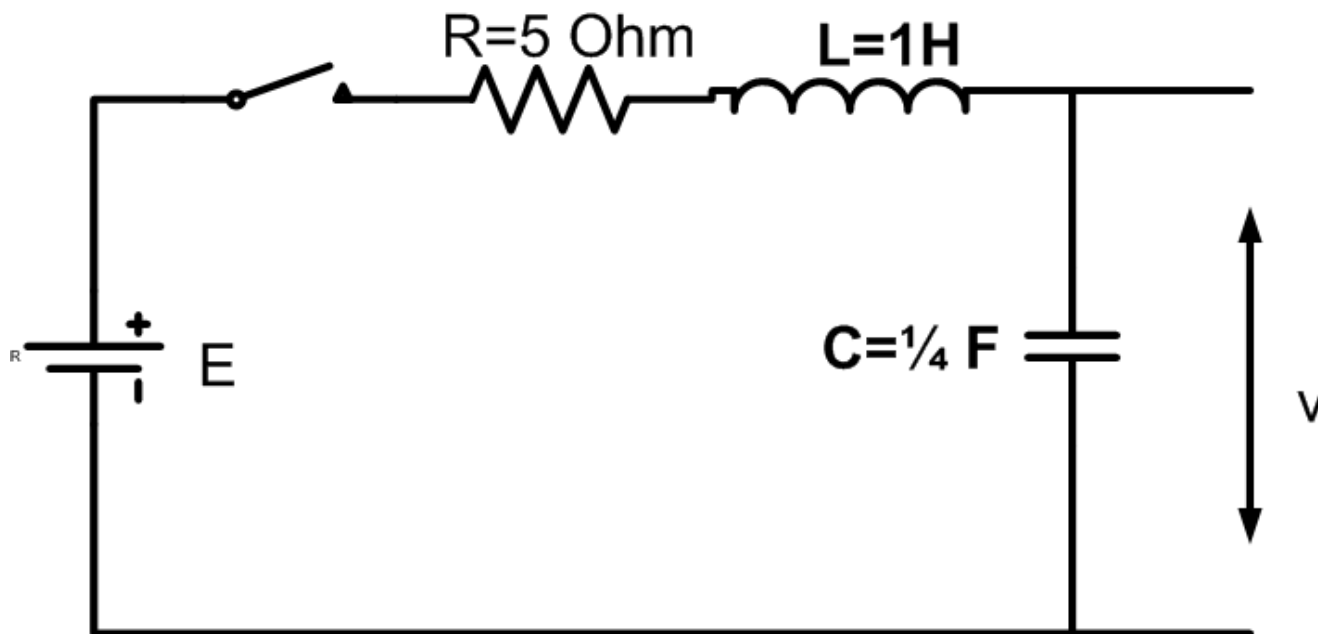


Fig.5: Network for the example



Example 1

- Consider the network shown in Fig.5. The differential equation governing the voltage V to the source E , is

$$v = \frac{\frac{1}{pC}}{R + pL + \frac{1}{pC}} = \frac{1}{p^2LC + pRC + 1} E = \frac{4}{p^2 + 5p + 4} E \quad (31)$$

- The associated differential equation is

$$\frac{d^2v}{dt^2} + 5 \frac{dv}{dt} + 4v = 4E \quad (323)$$

- The forced solution is

$$v_f = \frac{4}{p^2 + 5p + 4} \bigg|_{p=0} E = E \Rightarrow v_f = E \quad (33)$$

- The characteristics equation is

$$D(p) = D(s) = s^2 + 5s + 4 = (s + 4)(s + 1) = 0 \quad (34)$$



Example 1

- Hence

$$s_1 = -4, s_2 = -1$$

Hence, the complementary solution is

$$v_t = K_1 e^{-4t} + K_2 e^{-t}$$

Hence, the complete solution is

$$v = v_f + v_t = E + K_1 e^{-4t} + K_2 e^{-t} \quad (35)$$

- Since there are two unknown coefficients, two initial conditions are required. The first is that v has a zero value at time $t=0^+$, then

$$v(0^+) = 0 = E + K_1 + K_2 \quad (36)$$

- To determine the second initial condition, differentiate the eq. 35

$$\frac{dv}{dt} = -4K_1 e^{-4t} - K_2 e^{-t} \quad (37)$$





Example 1

- The term dv/dt is the voltage drop across the capacitor. At time $t=0+$, the voltage across the capacitor is zero because the inductor does not allow the current to flow the network immediately. Hence,

$$\begin{aligned}\frac{dv}{dt} &= -4K_1e^{-4t} - K_2e^{-t} = 0 \\ -4K_1 - K_2 &= 0\end{aligned}\tag{38}$$

- Solving eq.49 and eq.51 gives

$$K_1 = \frac{E}{3}, K_2 = -\frac{4}{3}E\tag{39}$$

- The complete solution is

$$v = E\left(1 + \frac{1}{3}e^{-4t} - \frac{4}{3}e^{-t}\right)\tag{40}$$





Example 1

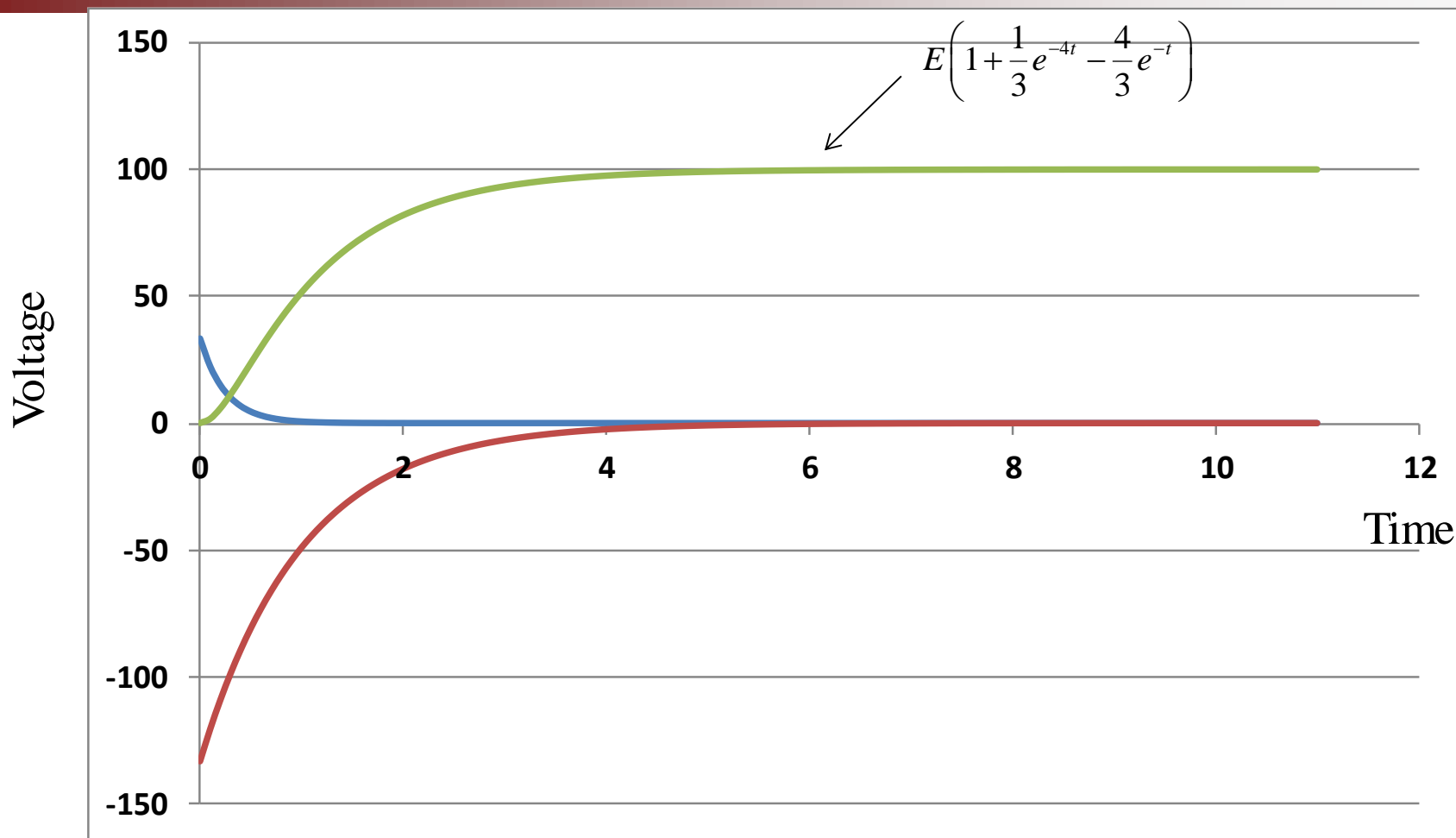


Fig.6: Response of network shown in fig.5



Example 2

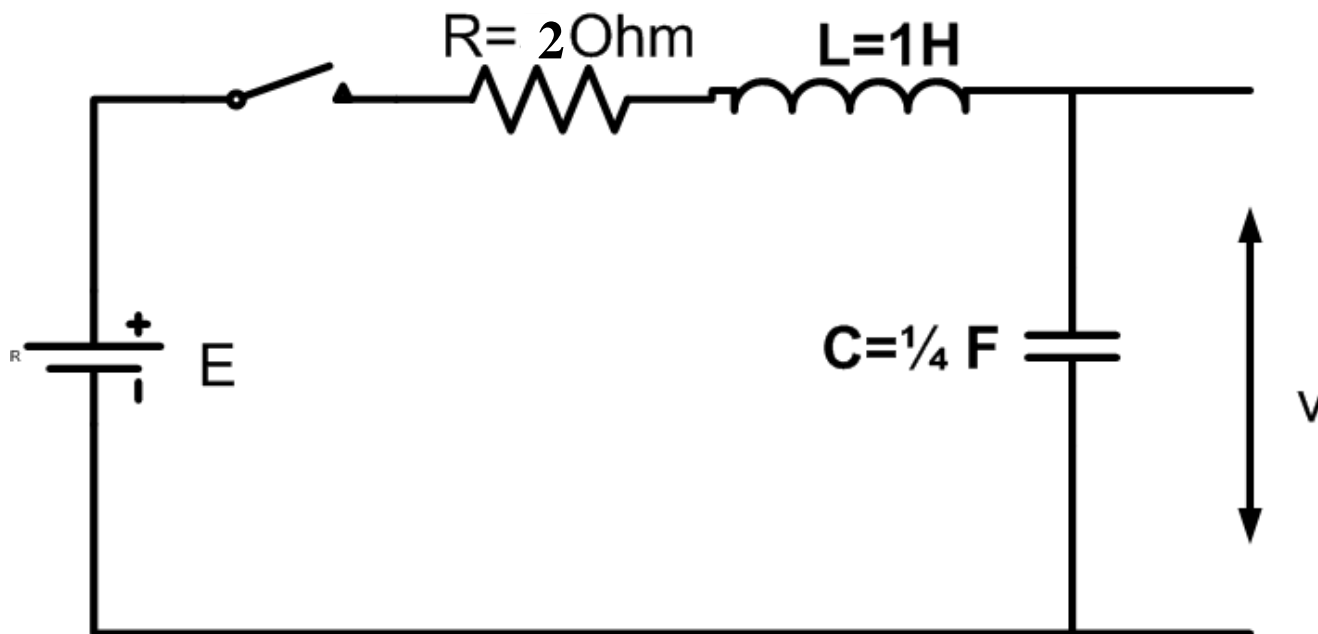


Fig.5: Network for the example



Example 2

- Consider the circuit shown in Fig. 7. The configuration of this circuit is same as in Fig.5 except for the fact that the resistance is reduced to 2 Ohms.

- The voltage v is given by

$$v = \frac{4}{p^2 + 2p + 4} E \quad (41)$$

- The forced component of the solution is obtained by

$$v_f = \frac{4}{p^2 + 2p + 4} \bigg|_{p=0} E = E \Rightarrow v_f = E \quad (42)$$

- The characteristic equation and its roots are

$$D(p) = D(s) = s^2 + 2s + 4 \quad (43)$$

$$s_1 = -1 + j\sqrt{3}$$

$$s_2 = -1 - j\sqrt{3}$$





Example 2

- It is important to note that the roots are no longer real and distinct but are complex conjugates.
- This should lead us to expect some essential difference in the behaviour of the circuit as it reacts to the application of the source function.
- This difference is seen by writing the expression for the transient response:

$$v_f = K_1 e^{s_1 t} + K_2 e^{s_2 t} = 1 / e^t \left(K_1 e^{i\sqrt{3}t} + K_2 e^{-j\sqrt{3}t} \right) \quad (44)$$

- Applying Euler's formula $e^{i\theta} = \cos \theta + j \sin \theta$, eq.44 can be written as

$$v_f = 1 / e^t \left[(K_1 + K_2) \cos \sqrt{3}t + j(K_1 - K_2) \sin \sqrt{3}t \right] \quad (45)$$

- It should be kept in mind that the left hand side of **eq.45** is a real quantity. Moreover, v_f is associated with a differential equation that has real coefficients.



Example 2

- Hence, the right hand side of eq.45 must also necessarily have real coefficients.
- This implies that the term $\mathbf{j}(\mathbf{K1-K2})$ merely means that $\mathbf{K1-K2}$ must assume such a value as to lead to a real coefficient.
- For ease of handling, the eq.45 can be rewritten as

$$v_f = 1 / e^t \left(k_1 \cos \sqrt{3}t + k_2 \sin \sqrt{3}t \right) \quad (46)$$

- The complete expression of the total solution is

$$v = E + v_f = E + 1 / e^t \left(k_1 \cos \sqrt{3}t + k_2 \sin \sqrt{3}t \right) \quad (47)$$

- Upon applying initial conditions to eq.47, the values of k_1 and k_2 can be obtained.





Example 2

- The first initial condition is

$$v(0^+) = 0 = E + k_1 \Rightarrow k_1 = -E \quad (48)$$

- To find k_2 , it is necessary to impose a second initial condition.

$$\frac{dv}{dt} = 0 = \sqrt{3}k_2 - k_1 \quad (49)$$

- Using eq.48, k_2 is found as

$$k_2 = \frac{k_1}{\sqrt{3}} = -\frac{E}{\sqrt{3}} \quad (50)$$

- Substituting k_1 and k_2 into eq.47 gives

$$v = E \left[1 - \frac{1}{e^t} \left(\cos \sqrt{3}t + \frac{1}{\sqrt{3}} \sin \sqrt{3}t \right) \right] \quad (51)$$

- The response of the system is shown in Fig.7



Example 2

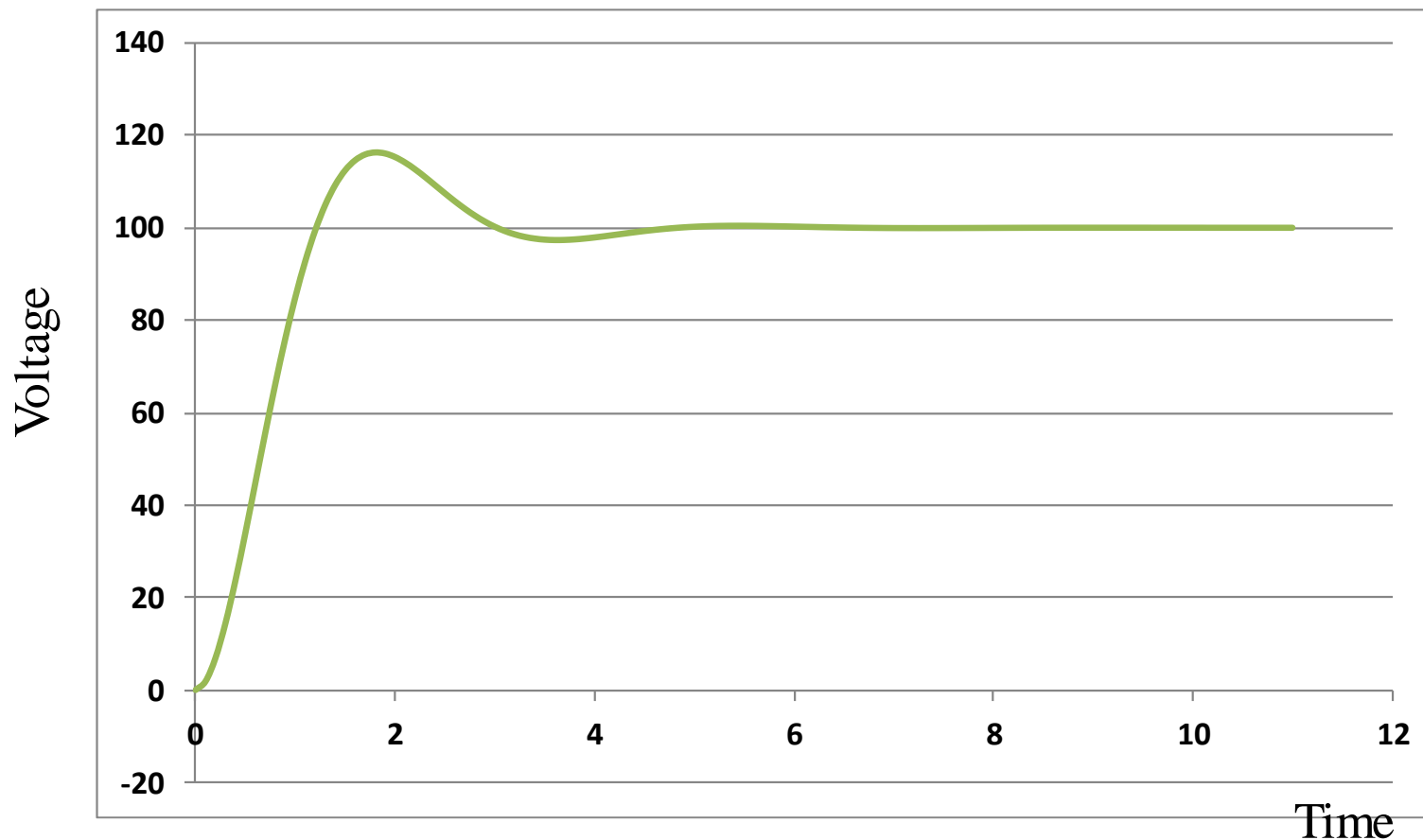


Fig.7: Response of network