


EE 101: Basic Electronics

Opamp and its applications


Nagarjuna Nallam

Department of EEE, IIT Guwahati, India

An opamp

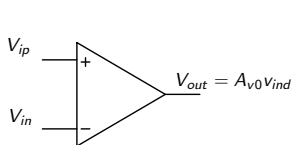

An opamp

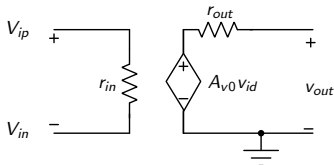

Equivalent model of an opamp

Differential input $V_{id} = V_{ip} - V_{in}$

Common-mode input $V_{ic} = \frac{V_{ip} + V_{in}}{2}$


For an ideal opamp

$$r_{in} = \infty$$


$$r_{out} = 0$$

$$A_{v0} \rightarrow \infty$$

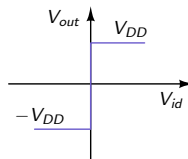
$$\text{Freq. Range is } 0 \rightarrow \infty$$



An ideal opamp

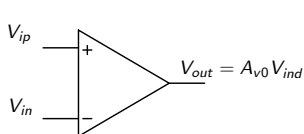

An ideal opamp

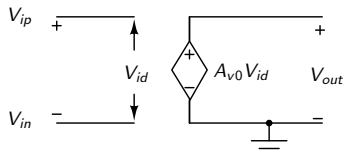


Macro model of an ideal opamp

Notes on ideal opamp:


1. Amplifies even differential DC signals (voltages)
2. Rejects all common-mode signals including DC voltages

An opamp circuit

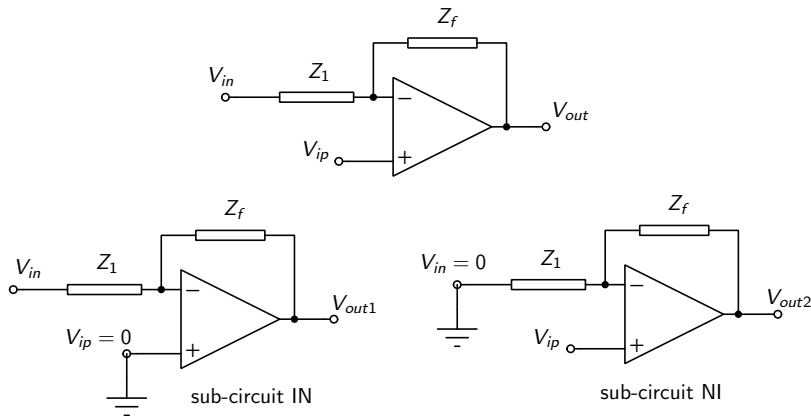

Superposition: $V_{out} = V_{out1} + V_{out2}$

Sub-circuit IN: Inverting Amplifier

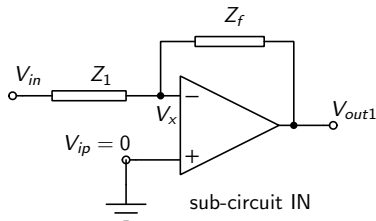

Let us assume the gain of the opamp $= A_v$

$$V_{out1} = A_v \times (0 - V_x) = -A_v V_x$$


$$\text{As } A_v \rightarrow \infty, V_x \rightarrow 0$$

No current flows into the opamp.

$$\frac{V_{in} - V_x}{Z_1} = \frac{V_x - V_{out1}}{Z_f}$$

$$\frac{V_{out}}{V_{in}} = -\frac{Z_f}{Z_1}$$

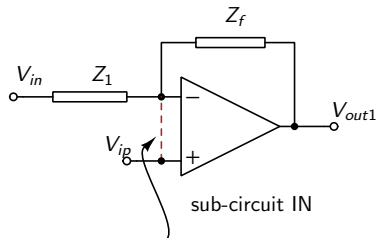Negative feedback: Virtual Short with no current




Virtual short for voltages (no current flows)




Only if the opamp is in negative feedback
and $A_v \rightarrow \infty$

Analysis of inverting amplifier

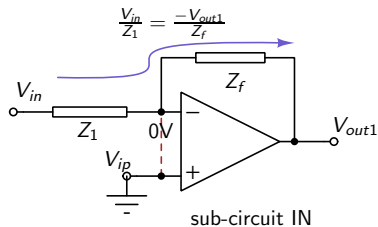


Analysis of non-inverting amplifier

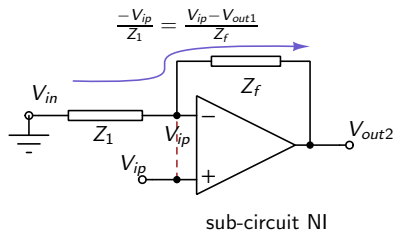


$$\text{Voltage gain } \frac{V_{out2}}{V_{ip}} = 1 + \frac{Z_f}{Z_1}$$


Opamp applications - 1

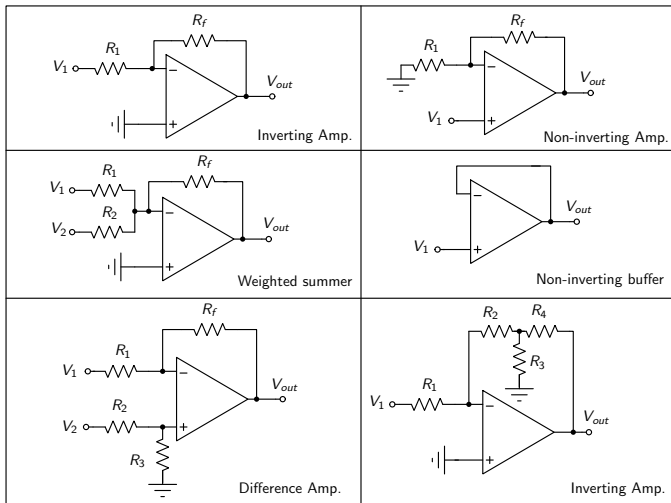

Opamp applications - 2

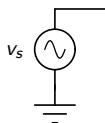


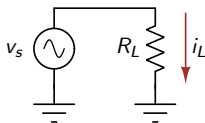Given a voltage signal,
how to convert it into a
current signal?




$$i_L = \frac{v_s}{R_L}$$

Larger the R_L , smaller is the i_L .

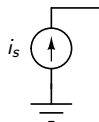

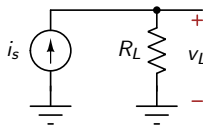
Given a current signal,
how to convert it into a
voltage signal?




$$v_L = i_L R_L$$

Smaller the R_L , smaller is the v_L .


Opamp applications - 2

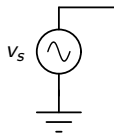

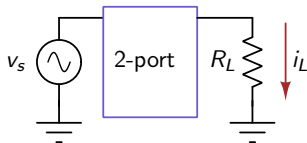
Given a voltage signal,
how to convert it into a
current signal?



i_L should be independent of R_L

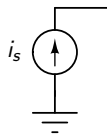

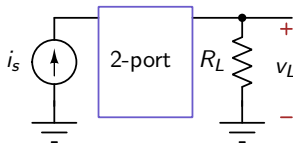
Given a current signal,
how to convert it into a
voltage signal?



v_L should be independent of R_L


Opamp applications - 2

V-I Converter

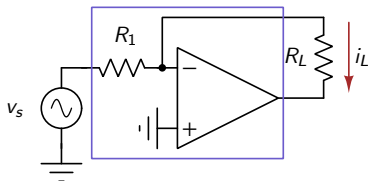

$$i_L = \frac{-v_s}{R_1} \text{ is independent of } R_L$$


I-V Converter

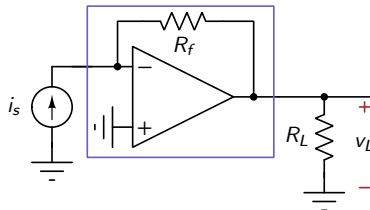

$$v_L = -i_s R_f \text{ is independent of } R_L$$


Opamp applications - 2

V-I Converter

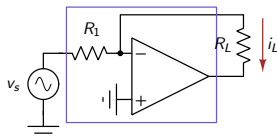


$$i_L = \frac{-v_s}{R_1} \text{ is independent of } R_L$$

I-V Converter

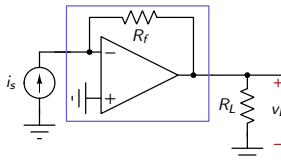


$$v_L = -i_s R_f \text{ is independent of } R_L$$

V-I Converter for grounded loads

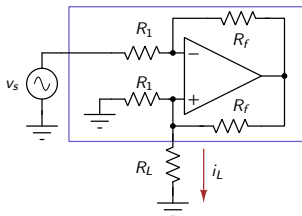

$$i_L = \frac{v_s}{R_1}$$


Current Amplifier

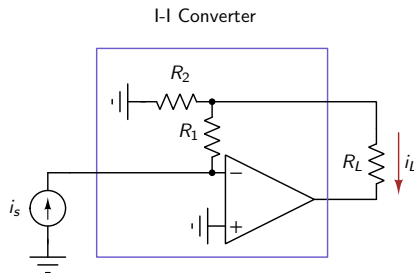



$$i_L = i_s + i_s \frac{R_1}{R_2} = \left(1 + \frac{R_1}{R_2}\right) i_s$$

A current amplifier: load current is independent of R_L .

Integrator

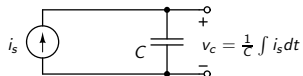


Analog Voltage Integration:

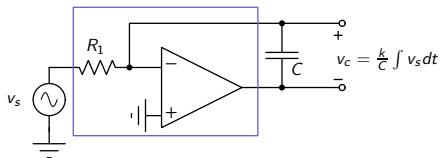
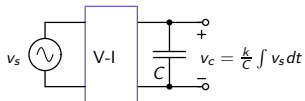


$$v_c = \frac{1}{R_1 C} \int v_s dt$$

Differentiator

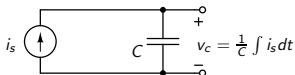


Analog Voltage Integration:

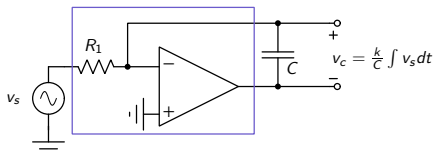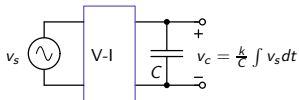

$$v_c = \frac{1}{R_1 C} \int v_s dt$$


Analog Voltage Differentiation:

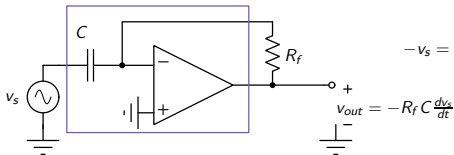

$$-v_s = \frac{1}{R_f C} \int v_{out} dt$$

Opamp applications - 2

Phase shifter:

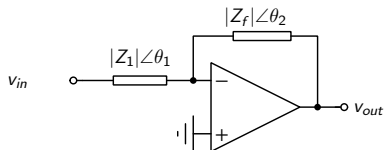

$$v_{out} = \left| \frac{Z_f}{Z_1} \right| \angle (\theta_2 - \theta_1) v_{in}$$

Opamp applications - Summary



1. Inverting and Non-inverting Amplifiers, Voltage buffer
2. Voltage Summer, Voltage subtractor
3. V-I converter or Transconductor or Voltage Controlled Current Source
4. I-V converter or Transresistor or Current Controlled Voltage Source
5. I-I converter or Current amplifier or Current Controlled Current Source
6. Voltage integrator
7. Voltage differentiator
8. Phase shifter

Further Learning ...

[1] A. Sedra and K. C. Smith, "Microelectronic Circuits," 6th Ed., Oxford university press, 2011.

Backup slides

Opamp applications - 1

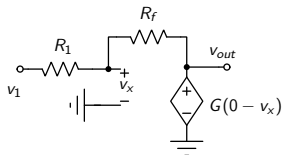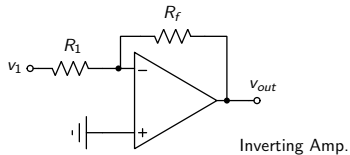



$$v_{out} = -Gv_x; \quad \frac{v_1 - v_x}{R_1} = \frac{v_1 - v_{out}}{R_1 + R_f}$$

$$\frac{v_1 + \frac{v_{out}}{G}}{R_1} = \frac{v_1 - v_{out}}{R_1 + R_f}$$

$$v_{out} = v_1 \frac{-R_f/R_1}{1 + \frac{R_1 + R_f}{GR_1}}$$

As $G \rightarrow \infty$,
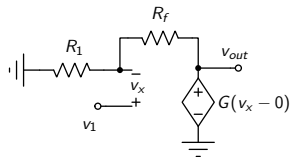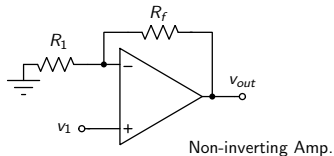
$$\frac{v_{out}}{v_1} = -\frac{R_f}{R_1}$$



$$v_{out} = Gv_x; \quad \frac{v_1 - v_x}{R_1} = \frac{v_{out}}{R_1 + R_f}$$



$$\frac{v_1 - \frac{v_{out}}{G}}{R_1} = \frac{v_{out}}{R_1 + R_f}$$

$$v_{out} = v_1 \frac{(R_f + R_1)/R_1}{1 + \frac{R_1 + R_f}{GR_1}}$$

As $G \rightarrow \infty$,



$$\frac{v_{out}}{v_1} = 1 + \frac{R_f}{R_1}$$

Opamp applications - 1

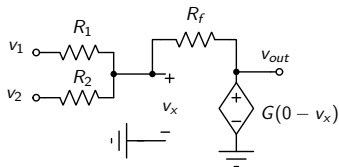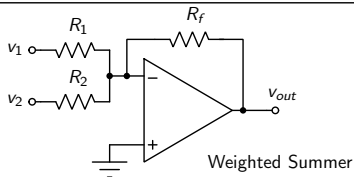

As $G \rightarrow \infty$,

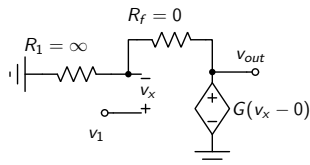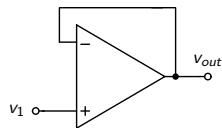
$$v_{out} = -\left[\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2\right]$$



As $G \rightarrow \infty$,

$$v_{out} = v_1$$

Opamp applications - 1

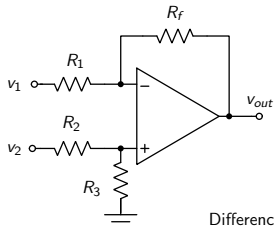


Difference Amp.

$$v_{out} = \frac{R_3}{R_2+R_3} \frac{R_1+R_f}{R_1} v_2 - \frac{R_f}{R_1} v_1$$

$$\text{If } \frac{R_3}{R_2} = \frac{R_f}{R_1},$$
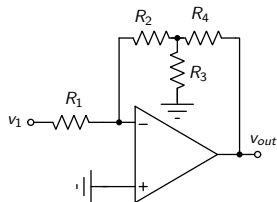
$$v_{out} = \frac{R_f}{R_1} (v_2 - v_1)$$



Inverting Amp.

?