

EE101:Electrical Sciences, Tutorial-9

DEPARTMENT OF ELECTRONICS & ELECTRICAL ENGINEERING

INDIAN INSTITUTE OF TECHNOLOGY GUWAHATI

[Q-1 is for pre-tutorial. Solve it in the space provided and submit at beginning of tutorial]

Name:

Roll No.:

Tutorial Group:

1. Two wattmeter method is employed to measure the 3-phase power. A 3-phase line supplies to a balanced inductive delta connected load. The current coil of Wattmeter W_1 is in line A and its voltage coil is connected across the line voltage V_{AC} . The current coil of Wattmeter W_2 is in line B and its voltage coil is connected across the line voltage V_{BC} . Derive the expressions for the readings of W_1 and W_2 in terms of the line voltage (V_L) and the line current (I_L) and the phase angle θ (angle between the phase voltage and phase current). Assume the line voltage V_{AB} as the reference. Draw the phasor diagram to explain your derivations.

Polyphase and Magnetic circuits

2. A 440 volt, 3-phase line supplies to an inductive delta connected load. Two wattmeter method is employed to measure the 3-phase power. If the two wattmeter readings are $W_1 = 15 \text{ kW}$ and $W_2 = 5 \text{ kW}$, find
 - (a) The line current
 - (b) The power factor
 - (c) Load resistance per phase and
 - (d) Load reactance per phase.

3. An electromagnet of square cross section ($2 \times 2 \text{ cm}^2$), shown in Fig.Q3(a), has a coil of $N=1300$ turns. The inner and the outer radii of the core are 10 cm and 12 cm respectively and the air gap length (l_g) is 1 cm. If the current in the coil is $i = 5 \text{ A}$ and the relative permeability of the core material is 1200, determine the flux density in the core.

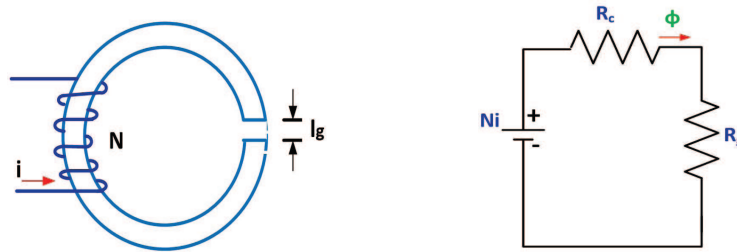


Fig.Q3(a):An electromagnet with air-gap Fig.Q3(b):Eq.magnetic circuit

Basic Electronics (Theme: Design with Macros)

4. LM35¹ is a low-cost precision centigrade temperature sensor with an analog output voltage proportional to the temperature in $^{\circ}\text{C}$. The transfer characteristics of the sensor are given by

$$V_{\text{OUT}} = 10 \text{ mV}/^{\circ}\text{C} \times T,$$

where V_{OUT} is the output dc voltage and T is the temperature in $^{\circ}\text{C}$. For example, the output voltage of the sensor at 25°C is 250 mV and at 100°C is 1000 mV. The sensor can detect the temperature in the range 10°C to 110°C . We want to interface it with a 10-bit Analog-to-Digital Converter (ADC) operating on a 5 V supply voltage. Design an ideal opamp based circuit that maps the output voltage of LM35 (that ranges from 0.1 V to 1.1 V) to the ADC full range (i.e., 0 V to 5 V).

HINT: First find out the transfer function of the circuit that you want to realize.

¹Why not do an online search about LM35? If possible, see the data sheet once.