

Tutorial-6 (Solutions)

Q-1:

 


Fig. 1a

Applying mesh analysis, for mesh 1

$$I_1 = 4A \quad (1)$$

For mesh 2,

$$(j10 - j5)I_2 - j10I_1 + 60\angle 30^\circ = 0 \quad (2)$$

Solving eq.1 and eq.2 gives

$$I_2 = -12\angle -60^\circ + 8 = 10.58\angle 79.1^\circ A \quad (3)$$

- a. For the current source, the current through it is $I_1 = 4\angle 0^\circ A$ and the voltage across it is:

$$V_1 = 20I_1 + j10(I_1 - I_2) = 183.9 + j20 = 184.984\angle 6.21^\circ V$$

The average power supplied by the current source is

$$P_1 = \frac{1}{2} (184.984) \times (4) \times \cos(6.21^\circ - 0^\circ) = 367.8W$$

- b. The current through the voltage source is:

$$I_2 = -12\angle -60^\circ + 8 = 10.58\angle 79.1^\circ A$$

The power delivered by the voltage source is

$$P_2 = \frac{1}{2} \times 10.58 \times 60 \times \cos(30^\circ - 79.1^\circ) = 207.8W$$

In view of the direction of I_2 and the polarity of the voltage source, the circuit is delivering average power to the voltage source.

- c. For the resistor, the current through it is I_1 and the voltage across it is $20 I_1$. Hence,

$$P_3 = \frac{1}{2} \times 80 \times 4 = 160W$$

d. For the inductor, the current through it is $I_1 - I_2 = 10.58 \angle -79.1^\circ$

The voltage across it is $j10(I_1 - I_2) = 10.58 \angle -79.1^\circ + 90^\circ$

hence, the average power absorbed by inductor is

$$P_4 = \frac{1}{2} \times 105.8 \times 10.58 \times \cos(90^\circ) = 0$$

e. For the capacitor, the current through it is I_2 and the voltage across it is $-j5I_2 = 52.9 \angle 79.1^\circ - 90^\circ$. The average power absorbed by the capacitor is

$$P_5 = \frac{1}{2} \times 52.9 \times 10.58 \times \cos(-90^\circ) = 0$$

Q-2: The impedance seen by the load is: $Z = 2j + \frac{(2 + 2j)(-2j)}{2} = 2\Omega$

For maximum power transfer, the load impedance should be 2Ω

Q-3:

 


Fig. 3a

V_{th} : Using source transformation, we get,

 


Fig. 3b

$$I = \frac{100 - (j0.2V_x)}{20 - j10} = \frac{100 + j0.2V_x}{20 - j10}$$

Applying KVL for circuit shown in Fig. 3b -

- $100 - V_x - I(-j10) - (-j0.2V_x) = 0$
 $\Rightarrow 100 - V_x + \left(\frac{100 + j0.2V_x}{20 - j10} \right) (j10) + j0.2V_x = 0$
 $\Rightarrow (100 - V_x)(20 - j10) + j1000 - 2V_x + j0.2V_x(20 - j10) = 0$

$$\Rightarrow 2000 - j1000 - 20V_X + j10V_X + j1000 - 2V_X + j4V_X + 2V_X = 0$$

$$\Rightarrow V_X = 67.11 + j46.98 = 81.92\angle 35^\circ$$

- $V_{th} = 100\angle 0^\circ - V_X = 100\angle 0^\circ - (81.92\angle 35^\circ)$

$$\Rightarrow V_{th} = 32.89 - j46.98 = 57.35\angle -55^\circ \text{ V}$$

 


Fig. 3c

- As shown in Fig. 3c, $I_{SC} = \frac{100}{20} + 0.02V_X = 5 + 0.02(100) = 7 \text{ A}$

- $Z_{th} = \frac{V_{th}}{I_{SC}} = 57.35\angle -55^\circ / 7 \Rightarrow Z_{th} = (4.699 - j6.711)\Omega$

- Thevenin's equivalent circuit (shown in Fig. 3d):

$$V_{th} = 57.35\angle -55^\circ \text{ V and, } Z_{th} = 4.699 - j6.711 \Omega$$

 


Fig. 3d

Q-4: It is clear that the clock signal arriving at the JK Flip-flop should be inverted before being connected to the T Flip-flop for the desired behaviour. Now, the table describing the transitions of the JK Flip-flop and the input to the T Flip-flop is as follows:

Q(k)	J	K	Q(k+1)	T
0	0	0	0	0
0	0	1	0	0
0	1	0	1	1
0	1	1	1	1
1	0	0	1	0
1	0	1	0	1
1	1	0	1	0
1	1	1	0	1

Fig. 4a. State transition of JK flip-flop

JK Q(k)		JK			
		00	01	11	10
0	0	0	0	1	1
	1	0	1	1	0

Fig. 4b. The Karnaugh map for T

The minimal SOP is: $T = JQ(k)' + KQ(k)$


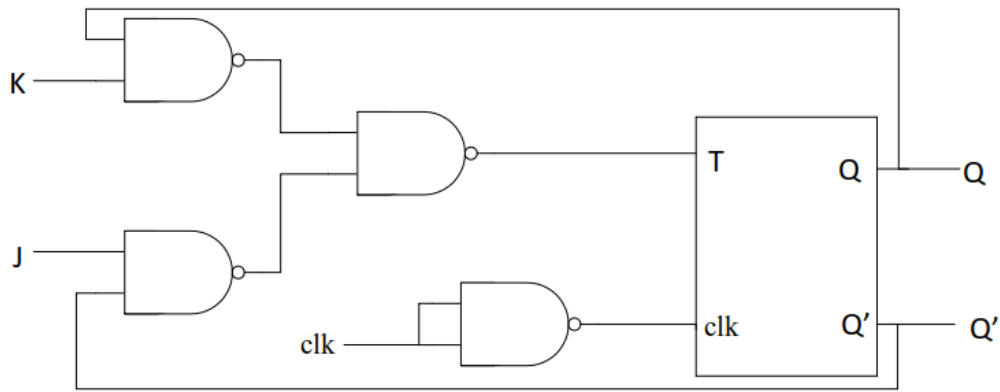


Fig. 4c. JK flip flop using positive edge triggered T flip-flop and NAND gates

Q-5: a)

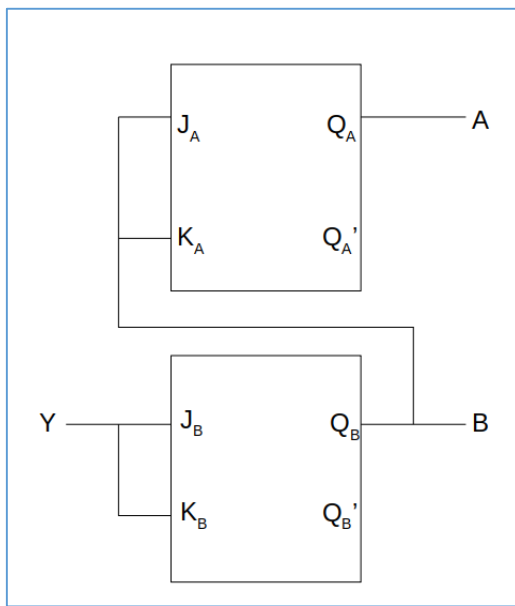

Present state		Input	Next state		Flip-Flop Inputs			
A	B	Y	A	B	J _A	K _A	J _B	K _B
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	1	1	X	X	0
0	1	1	1	0	1	X	X	1
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	0	1	X	1	X	0
1	1	1	0	0	X	1	X	1

Fig. 5. Sequential circuit using 2 JK flip-flops

Fig. 5a. JK flip-flop state table

b) To solve $A(t+1)$

Y \ AB				
	00	01	11	10
0	0	1	0	1
1	0	1	0	1

Fig. 5b.

$$A(t+1) = A'B + AB' = A \text{ XOR } B$$

To solve $B(t+1)$

Y \ AB				
	00	01	11	10
0	0	1	1	0
1	1	0	0	1

Fig. 5c.

$$B(t+1) = Y'B + YB' = Y \text{ XOR } B$$

c) To solve J_A

Y \ AB				
	00	01	11	10
0	0	1	X	X
1	0	1	X	X

Fig. 5d.

$J_A = B(t)$

To solve K_A

Y \ AB				
	00	01	11	10
0	X	X	1	0
1	X	X	1	0

Fig. 5e.

$K_A = B(t)$

To solve J_B

Y \ AB				
	00	01	11	10
0	0	X	X	0
1	1	X	X	1

Fig. 5f .

$J_B = Y(t)$

To solve K_B

Y \ AB				
	00	01	11	10
0	X	0	0	X
1	X	1	1	X

Fig. 5g.

$K_B = Y(t)$

Note: Characteristic table for JK flip-flop

Flip-Flop Input		Next State	
J	K	$Q(t+1)$	$Q'(t+1)$
0	0	$Q(t)$	$Q(t)$
0	1	0	1
1	0	1	0
1	1	$Q'(t)$	$Q(t)$

Fig. 5h.

Present State	Next State	Flip-Flop Input	
		J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Fig. 5i.

Q-6: The circuit takes 4-bit input word (X, Y, Z, P) with P as the least significant bit (LSB) and outputs '1' for inputs {0, 1, 3, 4, 5, 6, 7, 8, 9, A, B, D}

a)

XY \ ZP				
	00	01	11	10
00	1	1	1	
01	1	1	1	1
11		1		
10	1	1	1	1

Fig. 6a.

ZP \ XY				
	00	01	11	10
00	1	1		1
01	1	1	1	1
11	1	1		1
10		1		1

Fig. 6b.

b) Minimized SOP:

$$X'Z' + X'P + Z'P + X'Y + XY' \text{ OR}$$

$$X'Z' + Y'P + Z'P + X'Y + XY' \text{ OR}$$

$$Y'Z' + X'P + Z'P + X'Y + XY' \text{ OR}$$

$$Y'Z' + Y'P + Z'P + X'Y + XY'$$

c) Minimized POS: $(X' + Y' + P)(X' + Y' + Z')(X + Y + Z' + P)$