


EE 101: Basic Electronics


Introduction to Analog Signal Processing Circuits

Nagarjuna Nallam


Department of EEE, IIT Guwahati, India



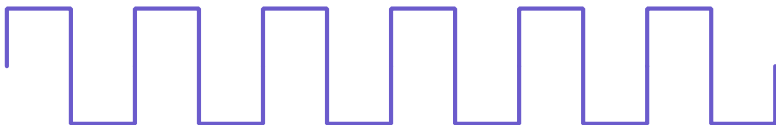


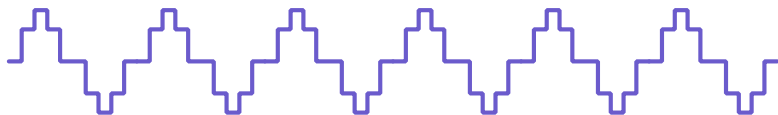


Signals: Analog, Discrete, Digital

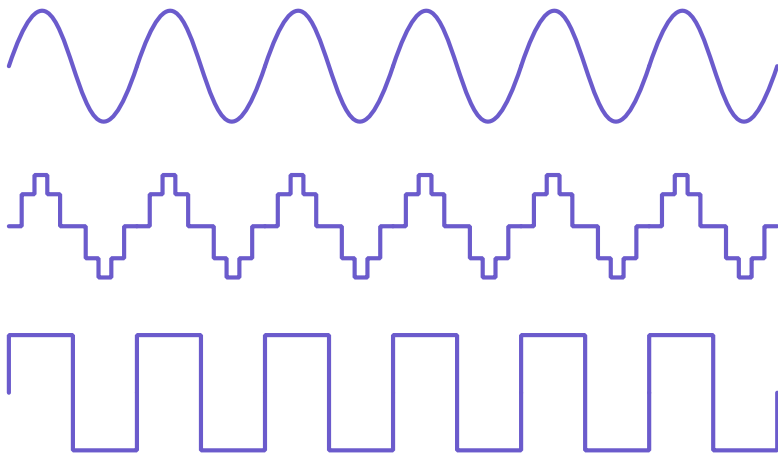


Signals: Analog, Discrete, Digital

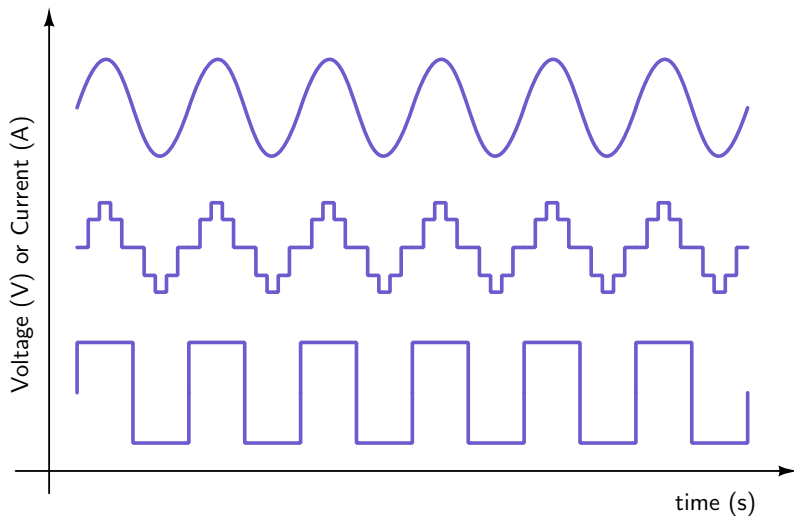

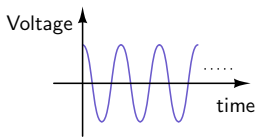
Conversion of a Signal: Analog→Discrete→Digital



Continuous-amplitude

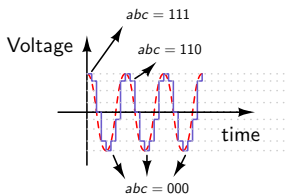


Discrete-amplitude

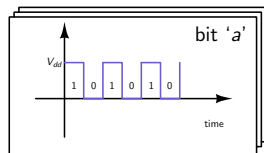

Digital signals (bits)

Analog and Mixed Signal Circuits

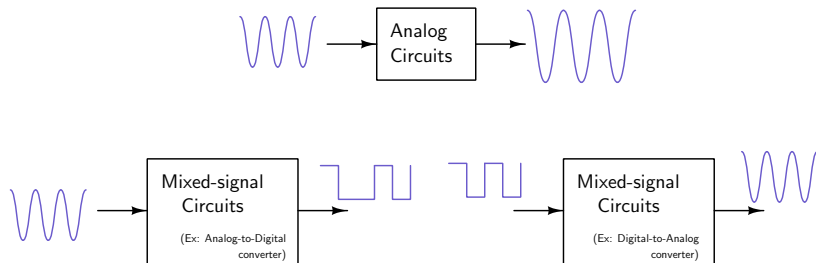


Why Analog?: Few articles to read

- ▶ “The World is Analog”
- ▶ “Engineering the world through Analog”
- ▶ “Connecting Bits to Life”
- ▶ “Secrets of the Universe - or - Look What Happened to Analog While Everyone Was Watching Digital”
- ▶ “Interesting fact: There is more analog in a digital handset than in an analog one”

Source:


http://www.ee.columbia.edu/~kinget/why_analog.html

Notation

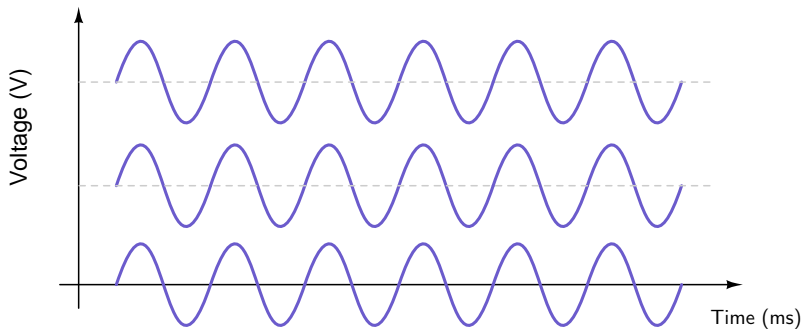


$$V_{in} = V_{IN} + v_{in} \sin(\omega t + \theta)$$


Identify the operation of the circuit

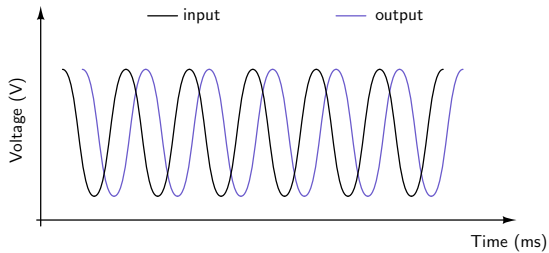


Identify the operation of the circuit

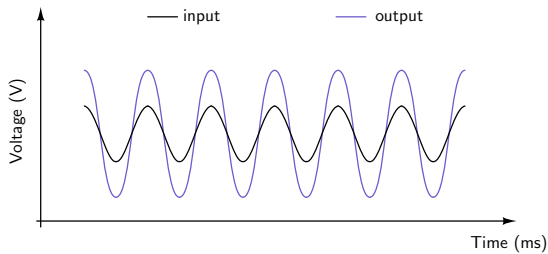


Identify the operation of the circuit

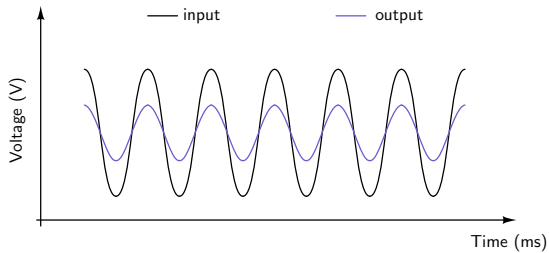


Identify the operation of the circuit

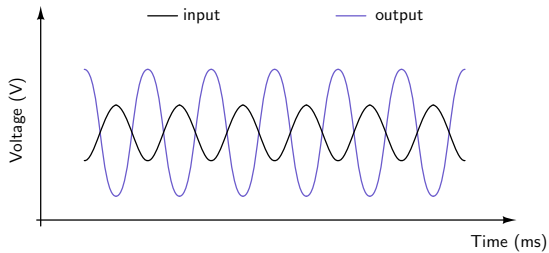


Identify the operation of the circuit

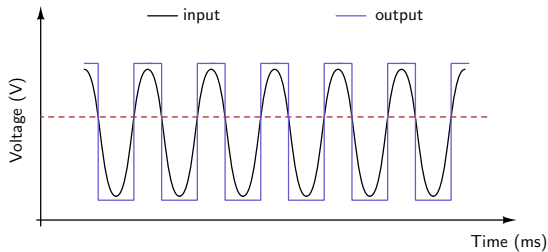


Identify the operation of the circuit

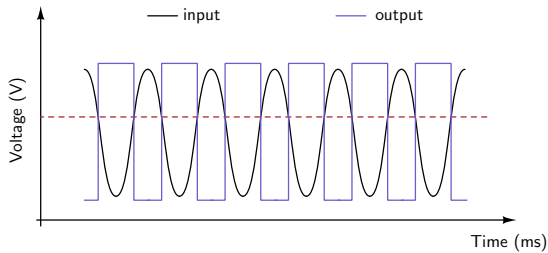


Identify the operation of the circuit

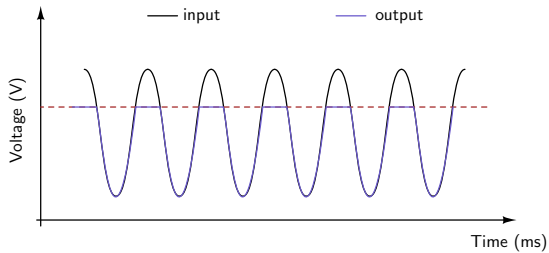


Identify the operation of the circuit

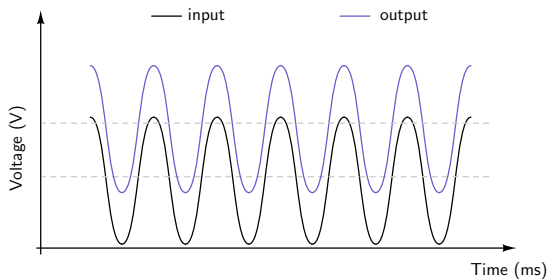

Identify the operation of the circuit

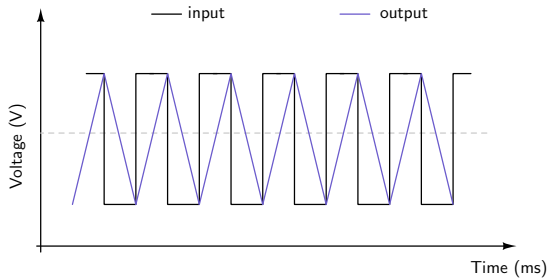

Identify the operation of the circuit

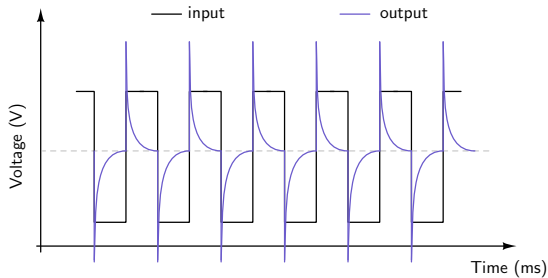

Summary

- ▶ Signals: Analog, Discrete, and Digital
- ▶ Notation: $V_{in}(t) = V_{IN} + v_{in}(t)$
- ▶ Signals: Variables or operands
- ▶ Circuits: Operators
- ▶ Circuits: What is the (transfer) function from input to output?

Reference Book

[1] A. Sedra and K. C. Smith, "Microelectronic Circuits," 6th Ed., Oxford university press, 2011.