



EE 101: Basic Electronics

BJT Amplifiers

Nagarjuna Nallam

Department of EEE, IIT Guwahati, India


Biasing

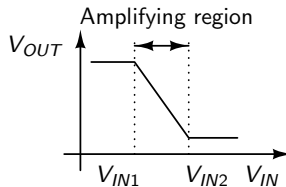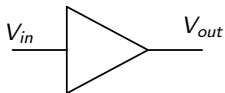

Input should have a DC offset within (V_{IN1} , V_{IN2})

What iff it is not the case?

AC-coupled amplifier


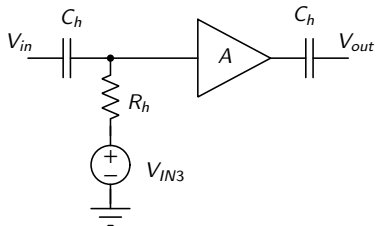


AC-coupled amplifier

C_h at the input blocks the DC in V_{in}



Amplifier can be biased at the max-gain point.

Amplifier gain for DC inputs is zero.

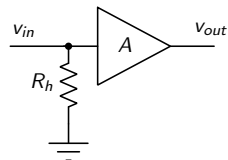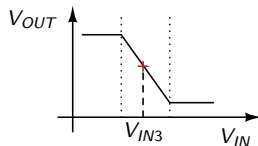


Mid-band equivalent circuit


Frequency Response

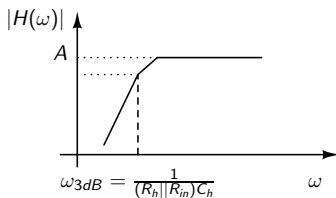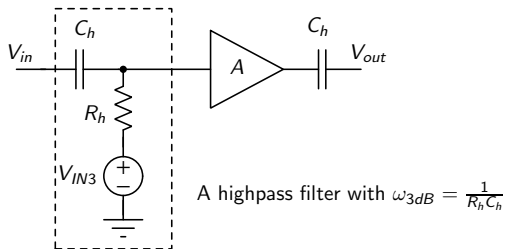


Biasing using a single supply

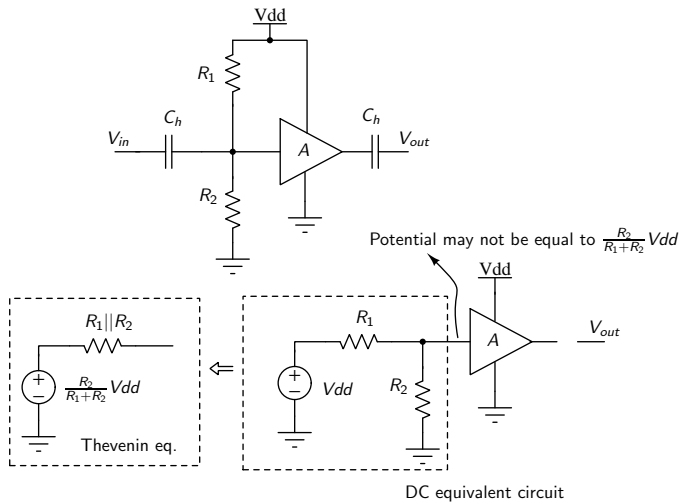


BJT configurations

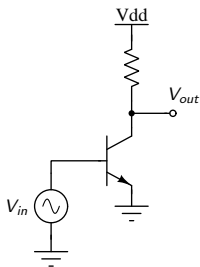

CE configuration

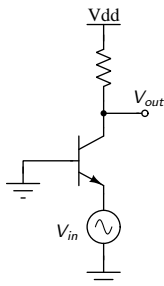

CB configuration

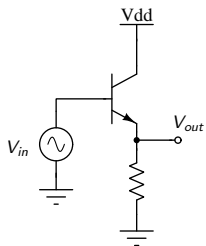


CC configuration



(Biasing is not shown in the above circuits)

Biasing a discrete CE amplifier


Biasing by I_B control

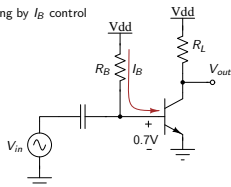

Biasing by V_{BB}

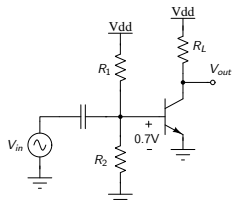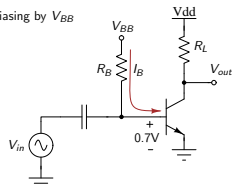


Biasing using a resistive divider

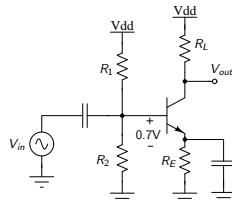


Biasing using an emitter degeneration resistor R_E

CE amplifier

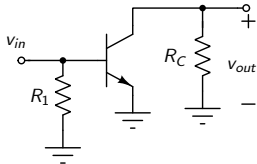

Typical AC equivalent circuit

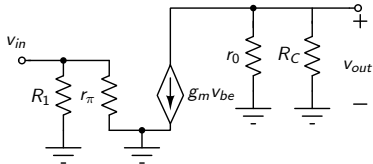


Small-signal model

$$\text{Input impedance} \approx R_1 \parallel r_{\pi}$$


$$\text{Output impedance} \approx r_0 \parallel R_C$$

$$\text{Voltage gain} \approx -g_m(r_0 \parallel R_C)$$


CE amplifier with emitter degeneration

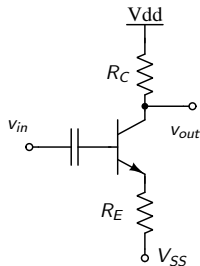

Circuit

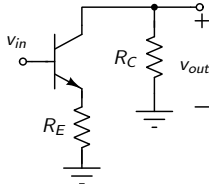

AC equivalent circuit

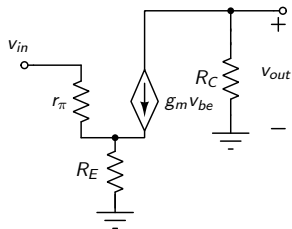


Small-signal model

$$\text{Input impedance} \approx r_{\pi} + (\beta + 1)R_E$$

$$\text{Output impedance} \approx R_C$$

$$\text{Voltage gain} \approx -\frac{g_m R_C}{1 + g_m R_E}$$

CB amplifier

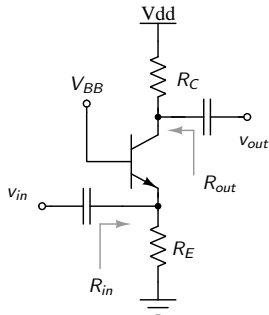


$$R_{in} \approx \frac{1}{g_m} \parallel R_E$$

$$R_{out} \approx r_o \parallel R_C$$

$$A_v \approx +g_m R_C$$

CC circuit

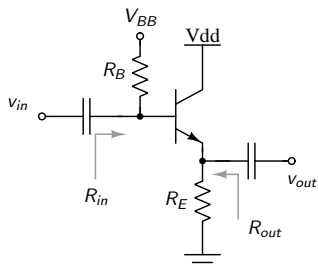

$$R_{in} \approx R_B || (r_{\pi} + (1 + \beta)R_E)$$

$$R_{out} \approx \frac{1}{g_m} || R_E$$

$$A_v \approx + \frac{g_m R_E}{1 + g_m R_E}$$

Summary

- ▶ DC and AC coupled amplifiers
- ▶ Biasing and frequency response of AC coupled amplifiers
- ▶ CE, CB and CC configurations
- ▶ CE amplifier: biasing, gain, input and output impedances
- ▶ CB amplifier: biasing, gain, input and output impedances
- ▶ CC buffer: biasing, gain, input and output impedances

Reference Book

[1] A. Sedra and K. C. Smith, "Microelectronic Circuits," 6th Ed., Oxford university press, 2011.