

Tutorial-2
EE 101: Electrical Sciences
DEPARTMENT OF ELECTRONICS & ELECTRICAL ENGINEERING
INDIAN INSTITUTE OF TECHNOLOGY GUWAHATI

*(First question is the **Pre-Tutorial Assignment problem** to be solved in the space provided.)*

Name:

Roll No.:

Tutorial Group:

1. Determine the voltages registered by a voltmeter between the following points in this circuit:

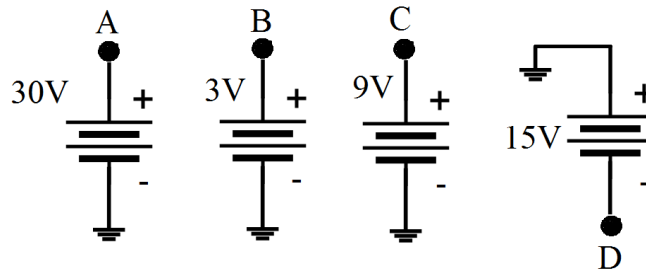


Fig. Q-1

a.	$V_A =$ (red lead on A, black lead on ground)
b.	$V_B =$ (red lead on B, black lead on ground)
c.	$V_C =$ (red lead on C, black lead on ground)
d.	$V_D =$ (red lead on D, black lead on ground)
e.	$V_{AC} =$ (red lead on A, black lead on C)
f.	$V_{DB} =$ (red lead on D, black lead on B)
g.	$V_{BA} =$ (red lead on B, black lead on A)
h.	$V_{BC} =$ (red lead on B, black lead on C)
i.	$V_{CD} =$ (red lead on C, black lead on D)

2. Use Kirchhoff's Voltage Law to calculate the magnitude and polarity of the voltage across resistor **R₄** in this resistor network (Fig. Q-2):

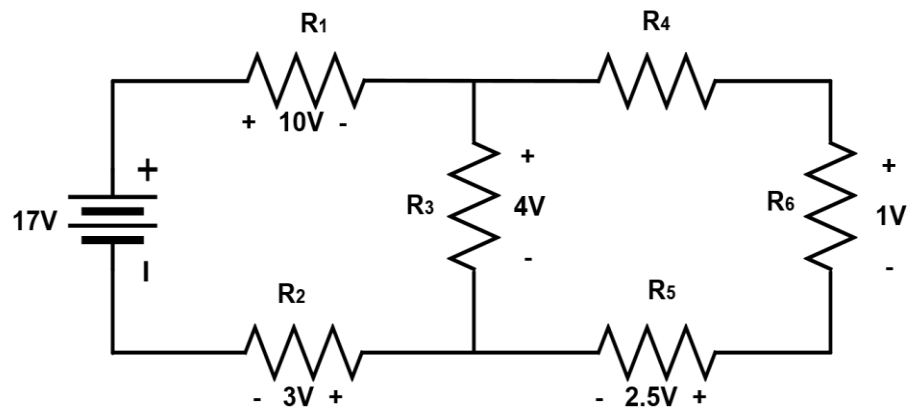


Fig. Q-2

3. Use Kirchhoff's Current Law to calculate the magnitudes and directions of currents through all resistors in this circuit (Fig. Q-3):

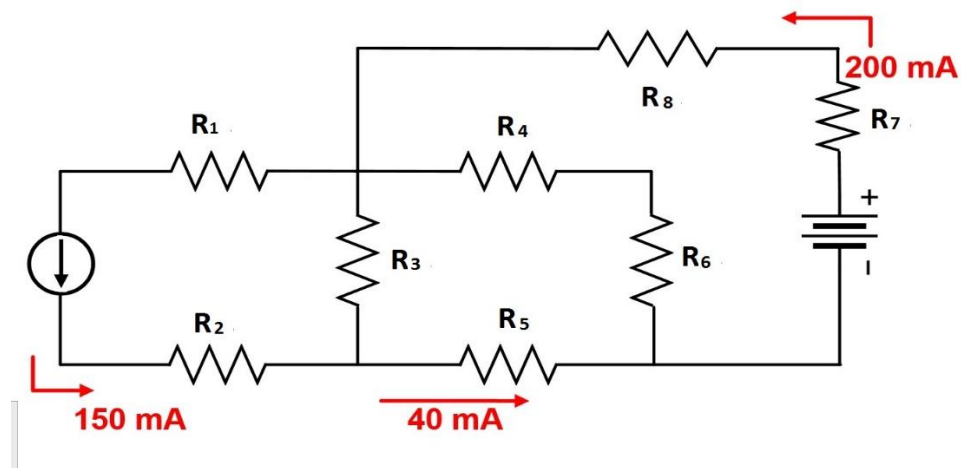


Fig. Q-3

4. Determine the current through **battery #2** in this power system, if the generator is outputting **50 amps**, **battery #1** is charging at a rate of **22 amps**, and the light bulbs draw **5 amps** of current each. Be sure to indicate whether battery #2 is charging or discharging (Fig. Q-4):

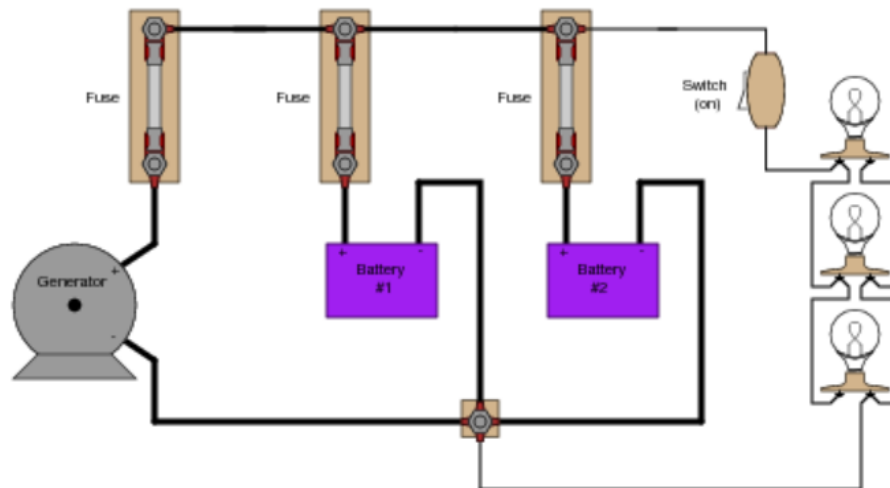


Fig. Q-4

5. Find the **decimal (base 10)** representation of the number $(1010101.111)_2$.
6. Find the **base 2** representation of the number $(43.6875)_{10}$.
7. Using identities of Boolean algebra, simplify the following expression as much as possible:

$$F(A, B, C, D) = \bar{A}B + B\bar{C} + BD + ABC\bar{D}$$

8. Using identities of Boolean algebra, simplify the following expression as much as possible:

$$F(A, B, C, D) = C\bar{D} + \bar{A}C + ABCD + A\bar{B}\bar{C}\bar{D}$$