





EE 101: Basic Electronics

Applications of Diodes





Nagarjuna Nallam

Department of EEE, IIT Guwahati, India





Half Wave Rectifier

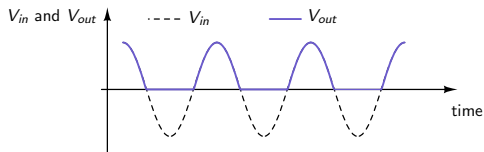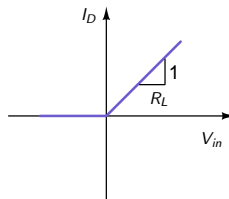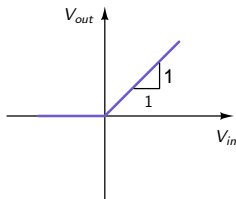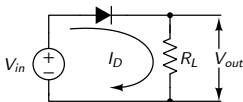




Half Wave Rectifier with a PN Diode

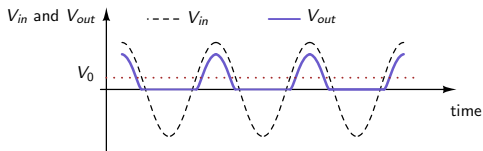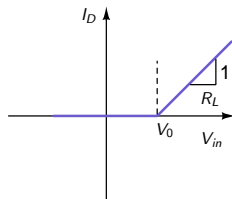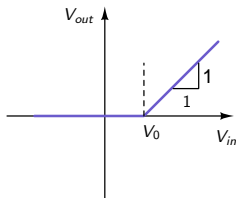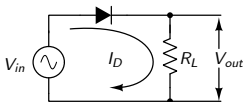




Half Wave Rectifier

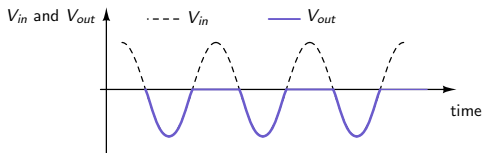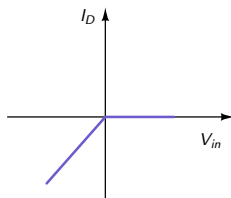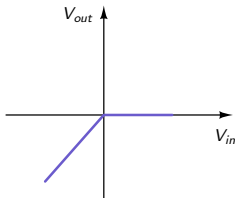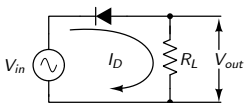



Full Wave Rectifier-1

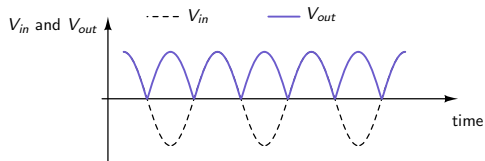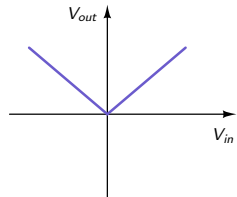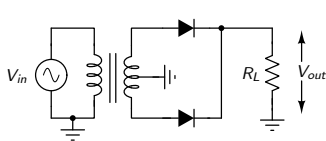

Full Wave Rectifier-2


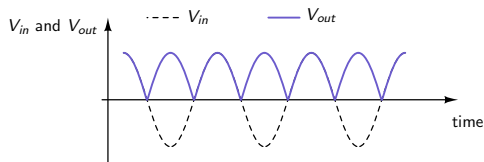
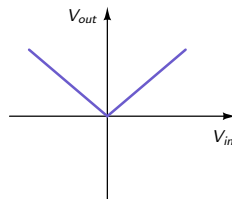
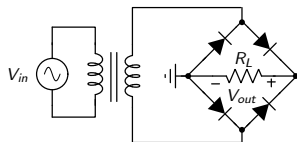


Peak Detector (AM Demodulator)

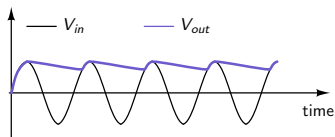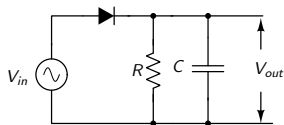


Only when $RC \gg$ Time period of the input voltage





Clippers

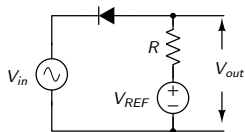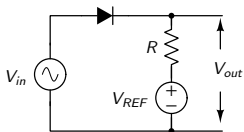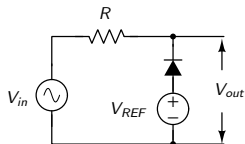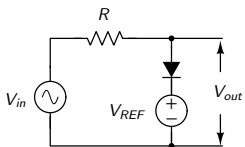


Two-sided Clipper

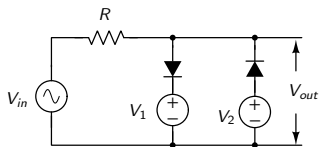


Clampers

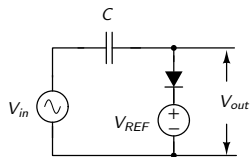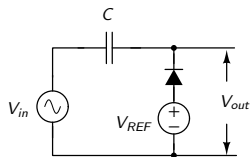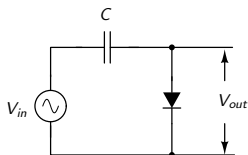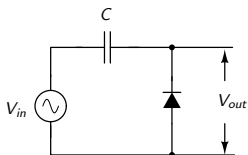

Voltage Doubler

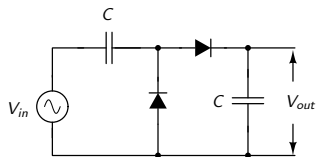


Voltage Regulation using Diodes

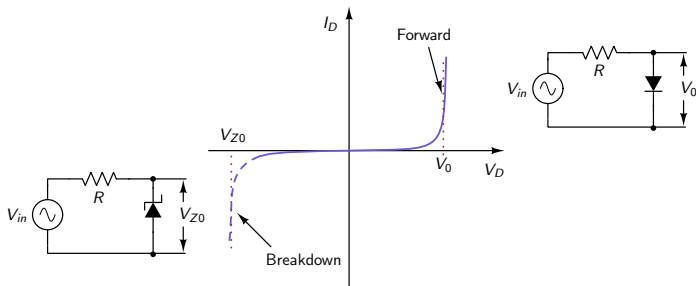

Zener diode: has low reverse breakdown voltage

Piecewise Linear Models

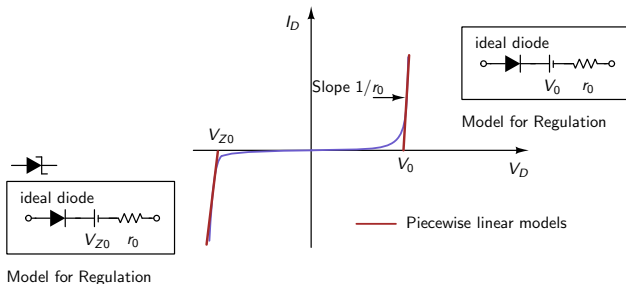

$$\text{Line Regulation} = \frac{\Delta V_{\text{Load}}}{\Delta V_{\text{IN}}}$$

$$\text{Load Regulation} = \frac{\Delta V_{\text{Load}}}{\Delta I_{\text{Load}}}$$

Summary

- ▶ Rectifiers
- ▶ Clippers
- ▶ Clampers
- ▶ Peak Detector
- ▶ Voltage doubler
- ▶ Voltage regulators

Reference Book

[1] A. Sedra and K. C. Smith, "Microelectronic Circuits," 6th Ed., Oxford university press, 2011.