

- Give answers neatly in the spaces provided.
- Answers must include appropriate SI units, where necessary.

Name:

Roll No:

Division:

Tutorial Group:

Q1. In the circuit shown in Fig.1, the values of the parameters are:

$$I_1 = 3A, R_1 = 3\Omega, R_2 = 2\Omega, V_1 = 4V, V_2 = 8V$$

What is the value of the current I ?

1 A

[2 marks]

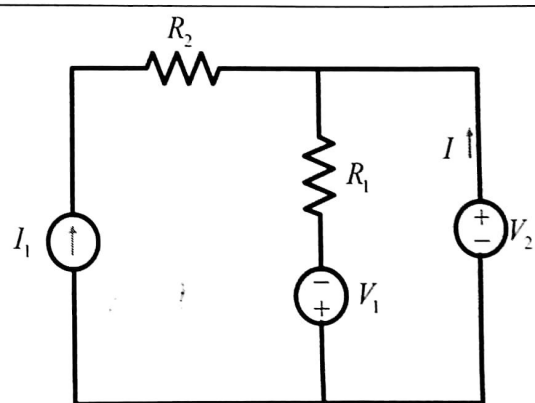


Fig.1: Figure for Q1.

Q2. In the circuit shown in Fig.2, the values of the parameters are:

$$V_{in} = 8V, R_1 = 1\Omega, R_2 = 2\Omega, R_4 = 0.5\Omega$$

For what value of R_3 will the power consumed by R_4 maximum?

0.5

[2 marks]

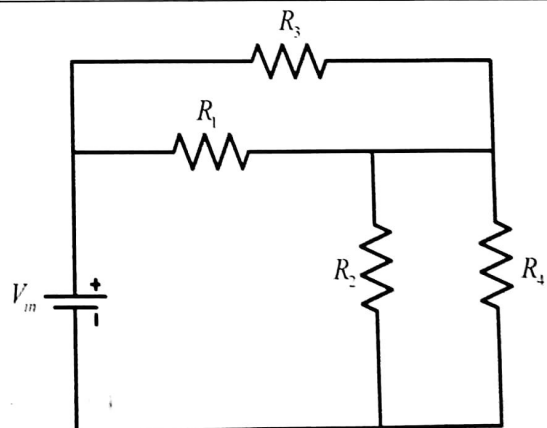


Fig.2: Figure for Q2.

Q3.(a) The base 2 representation of the number $\frac{45}{7}$ (expressed as a fraction in base 10) is

110.011

[1/2 mark]

Q3.(b) The base 10 representation of the number $(10011.101)_2$ is

19.625

[1/2 mark]

Q4. In the circuit shown in Fig.3, the values of the parameters are:

$$R_1 = 2\Omega, R_2 = 1\Omega, \alpha = 1$$

What is the value of V_2 / V_1 ?

0.5

[1 mark]

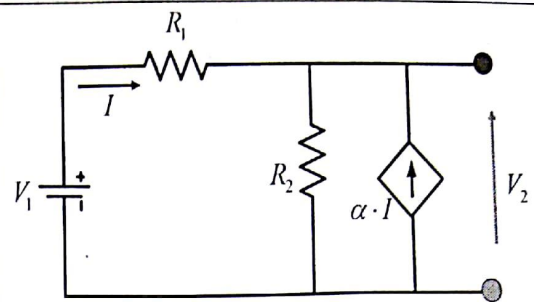


Fig.3: Figure for Q4.

Q5. Consider the logic circuit shown in Fig.4.

The minimal POS form is

$$F = (P + Q + R)(\bar{P} + \bar{Q} + \bar{R})$$

A minimal SOP form is

$$F = \bar{P}Q + \bar{Q}R + P\bar{R}$$

[2 marks]

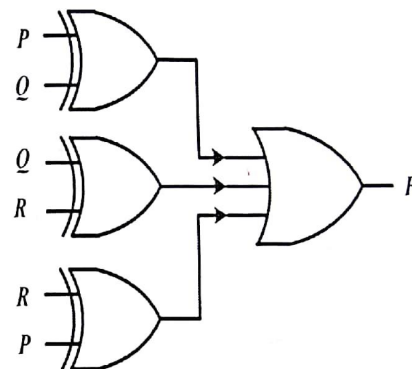


Fig.4: Figure for Q5.

Q6. Consider logic function described by the Boolean expression

$$F = (P + Q)(R + S) + (P + R)(Q + S) + (P + S)(Q + R)$$

The minimal SOP form of F is

$$F = PQ + PR + PS + QR + QS + RS$$

The minimal POS form of F is

$$F = (P + R + S)(P + Q + R)(P + Q + S)(Q + R + S)$$

[2 marks]