

## Solutions: Tutorial-5

Q-1.

A	B	C	D	S <sub>1</sub>	S <sub>0</sub>	I <sub>0</sub>	I <sub>1</sub>	I <sub>2</sub>	I <sub>3</sub>	F
0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	0	1	0	0	0	0
0	0	1	1	1	1	1	0	0	0	0
0	1	0	0	0	0	0	1	0	0	0
0	1	0	1	0	1	0	1	0	0	1
0	1	1	0	1	0	0	1	0	0	0
0	1	1	1	1	1	0	1	0	0	0
1	0	0	0	0	0	0	0	1	0	0
1	0	0	1	0	1	0	0	1	0	0
1	0	1	0	1	0	0	0	1	0	1
1	0	1	1	1	1	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	0	1	0	1	0	0	0	1	0
1	1	1	0	1	0	0	0	0	1	0
1	1	1	1	1	1	0	0	0	1	1

a. The Karnaugh map is:

		CD			
		00	01	11	10
AB	00	1	0	0	0
	01	0	1	0	0
	11	0	0	1	0
	10	0	0	0	1

b. The minimal SOP form:

$$= A'B'C'D' + A'BC'D + ABCD + AB'CD'$$

c. The minimal POS form:

$$= (A' + C)(A + C')(B' + D)(B + D')$$

**Q-2.**

<b>a.</b>	<b>b.</b>	<b>c.</b>	<b>d.</b>	<b>e.</b>
$i(0^+) = 0A$	$\frac{di}{dt}(0^+) = \frac{10}{L} = 10A/s$	$\frac{d^2i}{dt^2}(0^+) = -1000A/s^2$	$V_c(0^+) = 0V$	$V_L(0^+) = 10V$

**Q-3.**

- a.** If the switch is closed a long time before  $t=0$ , it means that the circuit has reached dc steady state at  $t=0$ . At dc steady state, the inductor acts like a short circuit, while the capacitor acts like an open circuit (Fig.3a). Hence, at  $t=0^-$ ,

$$i(0^-) = \frac{12}{4+2} = 2A, \quad v(0^-) = 2i(0^-) = 4V$$

Since the inductor current cannot change abruptly

$$i(0^+) = i(0^-) = 2A$$

- b.** From fig.5, and argument given in section **a**, the voltage is given by-

$$v(0^+) = v(0^-) = 4V$$

- c.** At time  $t=0^+$ , the switch is opened. The equivalent circuit is shown in (Fig.3b). The same current flows through both the inductor and capacitor. Hence,

$$i_c(0^+) = i(0^+) = 2A$$

Applying the KVL to the loop in Figure 2 results in

$$-12 + 4i(0^+) + v_L(0^+) + v(0^+) = 0$$

or

$$v_L(0^+) = 12 - 8 - 4 = 0$$

Hence,

$$\frac{di(0^+)}{dt} = \frac{v_L(0^+)}{L} = 0A/s$$

- d.** At time  $t=0^+$ , since

$$C \frac{dv}{dt} = i_c, \quad \frac{dv}{dt} = \frac{i_c}{C}$$

$$\frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = \frac{2}{0.1} = 20V/s$$

- e.**  $t \rightarrow \infty$ , the circuit reaches steady state, Fig.3c. The inductor acts like a short circuit and the capacitor like an open circuit, hence,  $i(\infty) = 0A$  and,
- f.**  $V(\infty) = 12V$ .

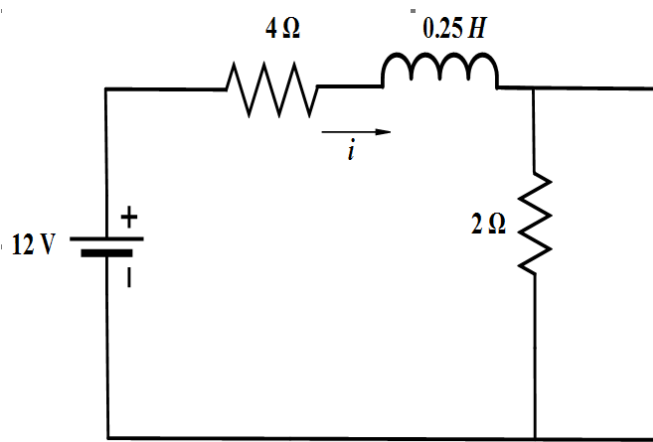


Fig.3a

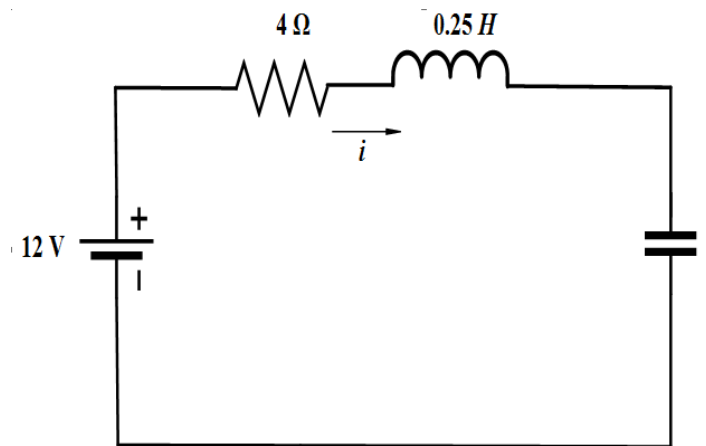


Fig.3b

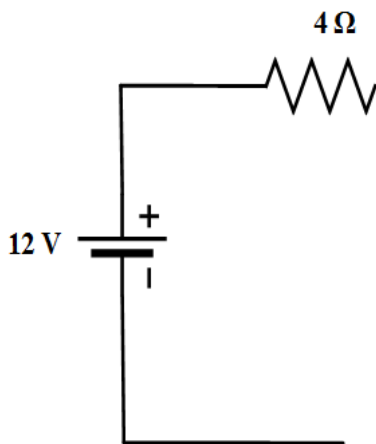


Fig.3c

**Q-4.** The operation impedances of the different branches are-

$$Z_R = 1$$

$$Z_L = 2p$$

$$Z_c = \frac{1}{pC} = \frac{3}{p}$$

The operation impedance of the as seen from the terminals **a-b** is-

$$Z_{ab} = Z_R + \frac{Z_L Z_c}{Z_L + Z_c} = 1 + \frac{2p \times \frac{3}{p}}{2p + \frac{3}{p}} = \frac{2p^2 + 6p + 3}{2p^2 + 3}$$

The current in the network is-

$$i = \frac{e}{Z_{ab}} = \frac{2p^2 + 3}{2p^2 + 6p + 3} e$$

the current through the inductor is

$$i_L = \frac{Z_C}{Z_L + Z_C} i = \frac{\frac{3}{p}}{2p + \frac{3}{p}} \times \frac{2p^2 + 3}{2p^2 + 6p + 3} e$$

$$= \frac{3}{2p^2 + 6p + 3} e$$

Hence, the governing differential equation is

$$(2p^2 + 6p + 3)i_L = 3e$$

$$\Rightarrow 2 \frac{d^2 i_L}{dt^2} + 6 \frac{di_L}{dt} + 3i_L = 3e$$

**Q-5.** The period of the waveform is  $T=4$ . Over a period, the current waveform can be written as-

$$i(t) = \begin{cases} 5t, & 0 < t < 2 \\ -10, & 2 < t < 4 \end{cases}$$

The rms value is

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = \sqrt{\frac{1}{4} \left[ \int_0^2 (5t)^2 dt + \int_2^4 (-10)^2 dt \right]}$$

$$= \sqrt{\frac{1}{4} \left[ 25 \frac{t^3}{3} \right]_0^2 + [100t]_2^4} = 8.165 A$$

The power absorbed by 2 Ohm resistor is

$$P = I_{rms}^2 R = (8.165)^2 (2) = 133.3 W$$

Q-6.

W	X	Y	Z	S	C	I <sub>0</sub>	I <sub>1</sub>	I <sub>2</sub>	I <sub>3</sub>	S <sub>1</sub>	S <sub>0</sub>	H
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	1	0	0	1	0	0	0	1	1
0	0	1	0	1	0	0	1	0	0	1	0	0
0	0	1	1	0	1	1	0	0	0	1	1	0
0	1	0	0	0	0	0	0	0	0	0	0	0
0	1	0	1	1	0	0	1	0	0	0	1	1
0	1	1	0	1	0	0	1	0	0	1	0	0
0	1	1	1	0	1	1	0	0	0	1	1	0
1	0	0	0	0	0	0	0	0	1	0	0	0
1	0	0	1	1	0	0	1	0	1	0	1	1
1	0	1	0	1	0	0	1	0	1	1	0	0
1	0	1	1	0	1	1	0	0	1	1	1	1
1	1	0	0	0	0	0	0	1	1	0	0	0
1	1	0	1	1	0	0	1	1	1	0	1	1
1	1	1	0	1	0	0	1	1	1	1	0	1
1	1	1	1	0	1	1	0	1	1	1	1	1

YZ \ WX				
	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	0	0	1	1
10	0	0	1	0

$$SOP: H = Y'Z + WZ + WXY \quad \text{and,}$$

$$POS: H = (Y + Z)(\overline{Y} + W)(X + Z)$$

Q-7.

X	Y	S <sub>1</sub>	S <sub>0</sub>	I <sub>0</sub>	I <sub>1</sub>	I <sub>2</sub>	I <sub>3</sub>	F
0	0	0	1	1	0	0	0	0
0	1	1	0	0	1	0	0	0
1	0	1	0	0	0	1	0	1
1	1	1	1	0	0	0	1	1

		X	
Y		0	1
	0	0	1
	1	0	1

$$F = X$$