

**EE101:Electrical Sciences, Tutorial-7**

DEPARTMENT OF ELECTRONICS & ELECTRICAL ENGINEERING

INDIAN INSTITUTE OF TECHNOLOGY GUWAHATI

[Q-1 is for pre-tutorial. Solve it in the space provided and submit at beginning of tutorial]

---

Name:

Roll No.:

Tutorial Group:

---

1. Write advantages / applications of a three phase network or circuit. Find the line voltages for a balanced three phase network if the phase voltages are given as  $v_{an} = V_P \sin(\omega t + 20^\circ)$ ,  $v_{bn} = V_P \sin(\omega t - 100^\circ)$  and  $v_{cn} = V_P \sin(\omega t - 220^\circ)$ . Draw the phasor diagram showing all the line and phase voltages.

## Polyphase Circuits

2. A balanced three-wire single phase system (Fig.Q2) has loads  $Z_{AN} = Z_{NB} = 10\Omega$  and a load  $Z_{AB} = 16 + j12\Omega$ . The three lines may be assumed to be resistanceless. If  $V_{an} = V_{nb} = 120\angle 0^\circ$  rms, find the currents  $I_{aA}$  and  $I_{nN}$ . If the system is made unbalanced by connecting another  $10\Omega$  resistance in parallel with  $Z_{AN}$ , find the currents  $I_{aA}$ ,  $I_{bB}$  and  $I_{nN}$ .

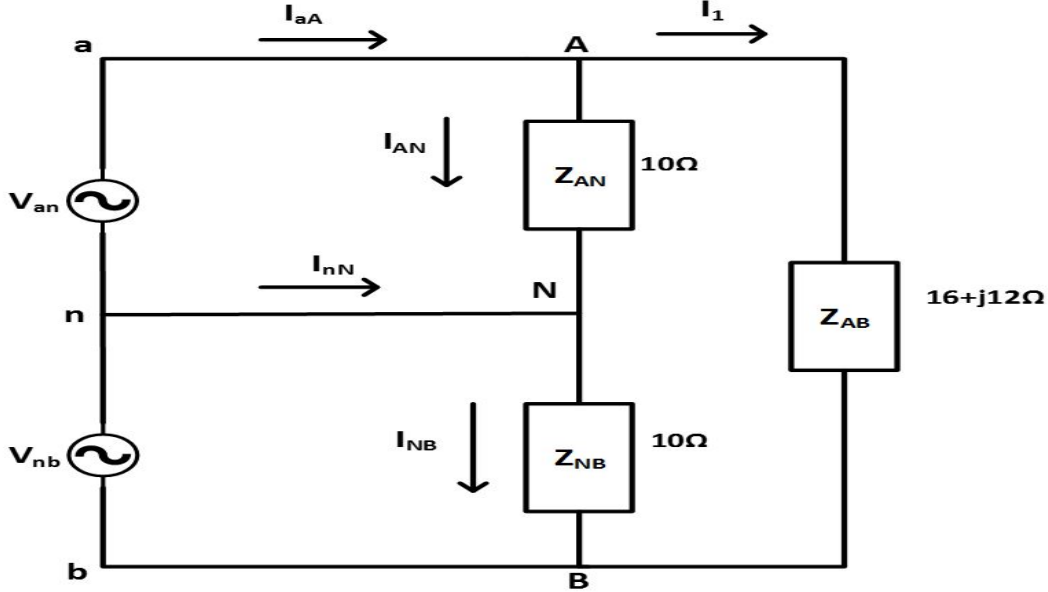


Fig.Q2

3. Three star connected impedances  $Z_1 = 20 + j37.7\Omega$  per phase are in parallel with three delta connected impedances  $Z_2 = 30 - j159.3\Omega$  per phase. The line voltage is 398 volts rms. Find the line currents, power factor, power and reactive volt ampere taken by the combination.

## Basic Electronics (Theme: Build with blocks)

4. A thermistor can be found in many (old) electronic appliances/systems. Some of its applications include (a) in fire alarm system (b) as a temperature detector in ovens, air-conditioners, etc. Design a block level fire alarm system that gets activated for temperatures above  $100^\circ\text{C}$  using the following components:
- A 9V battery
  - a  $103$  ( $10 \times 10^3\Omega$  at  $25^\circ\text{C}$ ) thermistor. Assume a linear variation in the resistance value with a temperature coefficient of  $-120\Omega/^\circ\text{C}$
  - other blocks/components required: comparator, an alarm/buzzer with an enable input, and  $10k\Omega$  resistors (only)
5. Convert the above system into a 4-bit temperature sensor. Procedure: Divide the temperature range between  $25^\circ\text{C}$  and  $100^\circ\text{C}$  into 16 levels (including  $25^\circ\text{C}$  and  $100^\circ\text{C}$ ) and assign a 4-bit code to each level starting from 0000 to 1111. Use 16 comparators with appropriate reference voltages to detect the temperature. Use a digital logic to encode the outputs of 16 comparators to 4-bits.