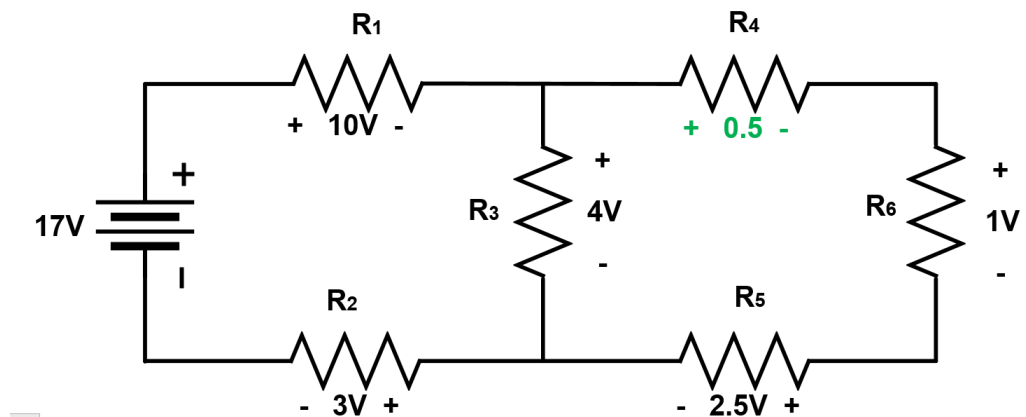


Tutorial-2: Solutions


Ans.1

- a. $V_A = +30$ volts (red lead on A, black lead on ground)
- b. $V_B = +3$ volts (red lead on B, black lead on ground)
- c. $V_C = +9$ volts (red lead on C, black lead on ground)
- d. $V_D = -15$ volts (red lead on D, black lead on ground)
- e. $V_{AC} = +21$ volts (red lead on A, black lead on C)
- f. $V_{DB} = -18$ volts (red lead on D, black lead on B)
- g. $V_{BA} = -27$ volts (red lead on B, black lead on A)
- h. $V_{BC} = -6$ volts (red lead on B, black lead on C)
- i. $V_{CD} = +24$ volts (red lead on C, black lead on D)

Ans.2



Ans.3

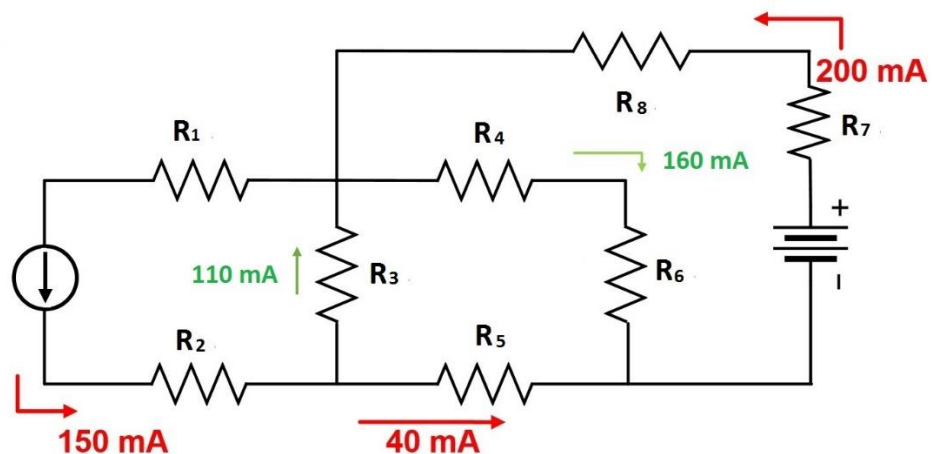

Ans.4

Battery #2 is charging at a rate of **13 amps**.

Ans.5

$$(1010101.111)_2$$

$$= 1 \times 2^6 + 0 \times 2^5 + 1 \times 2^4 + 0 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 + 1 \times 2^{-1} + 1 \times 2^{-2} + 1 \times 2^{-3}$$

$$= 64 + 16 + 4 + 1 + .5 + .25 + .125 = (85.875)_{10}$$

Ans. 6

$(43.6875)_{10}$

2	43	
2	21	1
2	10	1
2	5	0
2	2	1
2	1	0

$$(43)_{10} = (101011)_2$$

$$0.6875 \times 2 = 1.375$$

$$0.375 \times 2 = .750$$

$$0.75 \times 2 = 1.50$$

$$0.5 \times 2 = 1.0$$

$$\text{Thus, } (0.6875)_{10} = (.1011)_2$$

$$\mathbf{(43.6875)_{10} = (101011.1011)_2}$$

Ans. 7

$$\mathbf{F(A, B, C, D) = \bar{A}B + B\bar{C} + BD + ABC\bar{D}}$$

$$= B(\bar{A} + \bar{C} + D + AC\bar{D})$$

$$= B(\overline{AC} + D + AC\bar{D}); \text{ De Morgan's Law}$$

$$= B(\overline{AC} + D + AC); \text{ Absorption}$$

$$= B(1 + D) = B.1 = \mathbf{B}$$

Ans. 8

$$1 = A + \bar{A} = \bar{A} + A(B + \bar{B}) = \bar{A} + AB + A\bar{B}$$

$$\text{Thus, } C\bar{D} = C\bar{D}.1$$

$$= C\bar{D}(\bar{A} + AB + A\bar{B})$$

$$= \bar{A}C\bar{D} + ABC\bar{D} + A\bar{B}C\bar{D}$$

$$\mathbf{F(A, B, C, D) = C\bar{D} + \bar{A}C + ABCD + A\bar{B}\bar{C}\bar{D}}$$

$$= \bar{A}C\bar{D} + ABC\bar{D} + A\bar{B}C\bar{D} + \bar{A}C + ABCD + A\bar{B}\bar{C}\bar{D}$$

$$= \bar{A}C(1 + D) + ABC(D + \bar{D}) + A\bar{B}\bar{D}(C + \bar{C})$$

$$= \bar{A}C + ABC + A\bar{B}\bar{D}$$

$$= C(\bar{A} + AB) + A\bar{B}\bar{D}$$

$$= C(\bar{A} + B) + A\bar{B}\bar{D}$$

$$\mathbf{= \bar{A}C + BC + A\bar{B}\bar{D}}$$