

**Sol-1.**  $F(A, B, C, D) = \sum(6,9,10,11,14,15) + d(2,7,8,13)$

(a) : Minimal SOP form


Solution 1 :

Using red regions  $A\bar{B} + BC$

Or

Solution 2 :

Using blue regions  $C\bar{D} + AD$

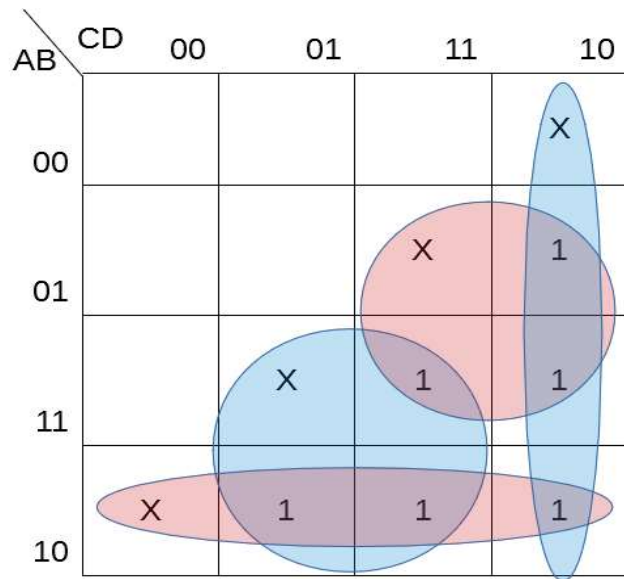

(b) : Minimal POS form


Solution 1 :

Using blue regions  $(A + B)(\bar{B} + C)$

Or

Solution 2 :

Using red regions  $(C + D)(A + \bar{D})$

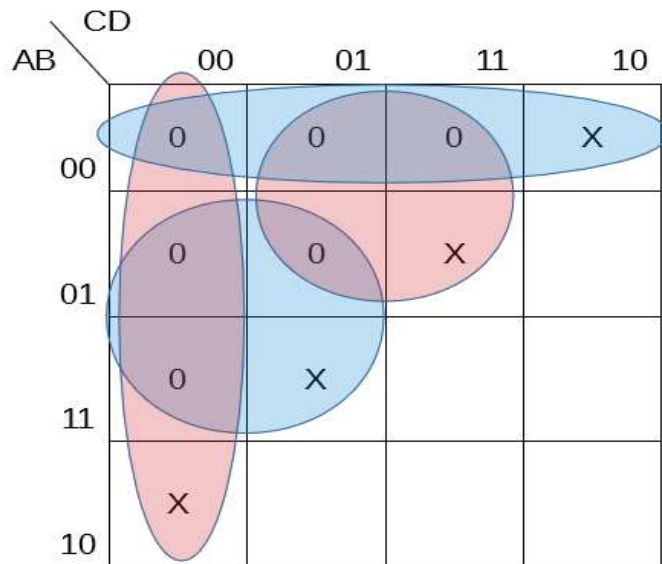

**Sol.2:**

**A) For Thevenin equivalent circuit:**

By Source transformation of 1A source,

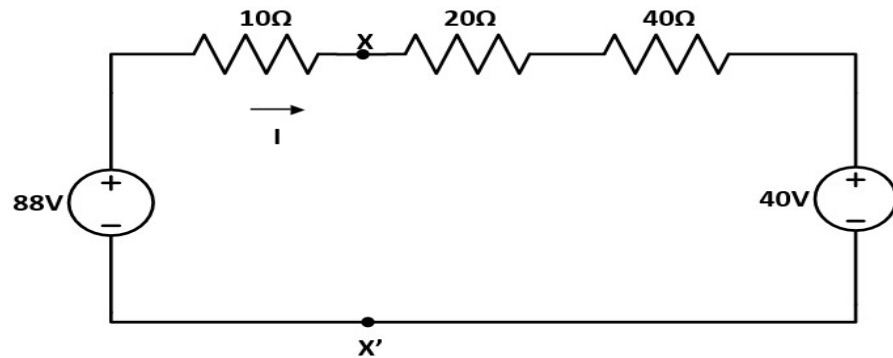


Fig. 1\_1

$$\Rightarrow I = \frac{88 - 40}{10 + 20 + 40} = 0.6857A$$

Voltage across  $X X' = V_{XX'} = 88 - 10 I$

$$= 88 - 10 \times 0.6857 = 81.143 \text{ V} \Rightarrow V_{TH} = V_{THEVENIN} = V_{XX'} = 81.143$$

**V.**

**For  $R_{TH}$ :** Deactivating the independent sources,

$$\Rightarrow 20 \Omega + 40 \Omega = 60 \Omega$$

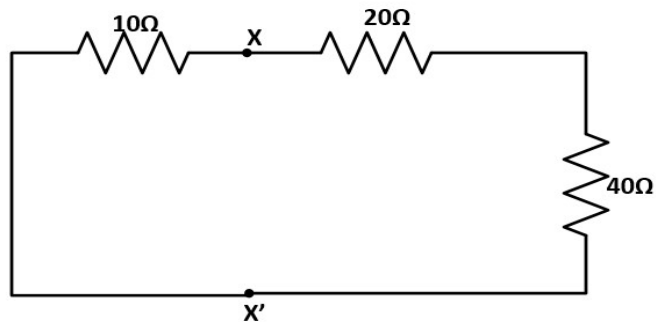


Fig. 1\_2

$$\Rightarrow R_{TH} = 10 \parallel 60 = 8.57 \Omega.$$

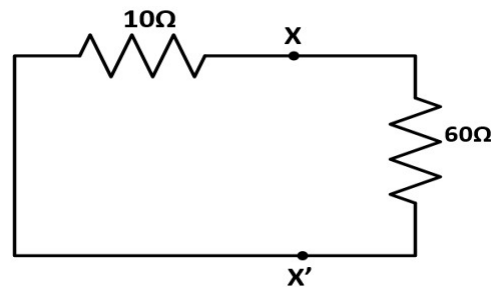


Fig. 1\_3

**Thevenin Equivalent Circuit:**

$$\text{Voltage across } xx' = V_{TH} \frac{50}{50+8.57}$$

$$= 81.143 \frac{50}{50+8.57} = \mathbf{69.27 \text{ V.}}$$

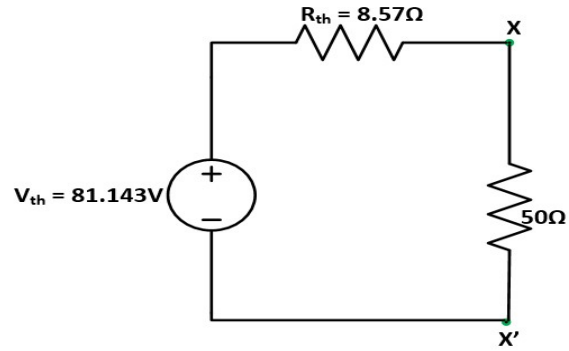


Fig. 1\_4

**B) For Norton's equivalent circuit:**

Using Source transformation of 1A source,

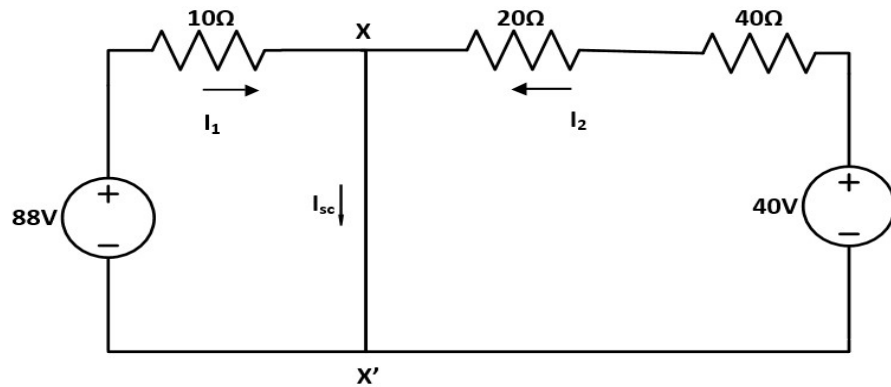


Fig. 1\_5

$[V_{xx'} = 0, \text{ as shortcircuit}]$

Now, Loop I  $\Rightarrow 88 - 10 I_1 = 0$

or,  $I_1 = \mathbf{8.8 \text{ A.}}$

Loop II  $\Rightarrow 40 - I_2 \times 60 = 0$

or,  $I_2 = \mathbf{0.67 \text{ A}}$

Now  $I_{SC} = I_1 + I_2 = \mathbf{9.47 \text{ A}}$

$R_{NORTON} = R_N$

$$\Rightarrow 20\ \Omega + 40\ \Omega = 60\Omega$$

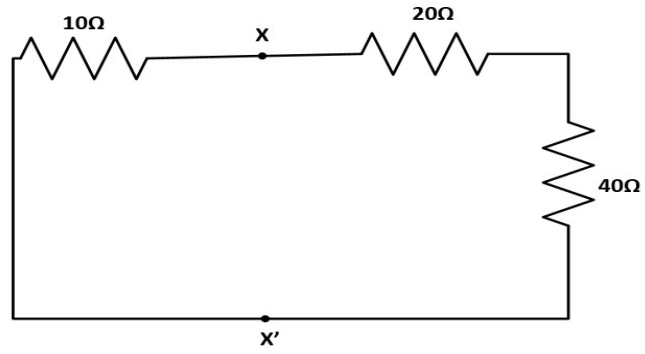


Fig. 1\_6

$$\Rightarrow R_{TH} = 10 \parallel 60 = 8.57\ \Omega.$$

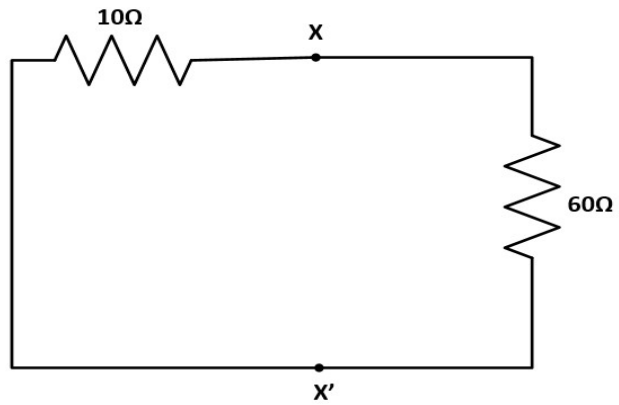


Fig. 1\_7

$\therefore$  Norton equivalent circuit is ,

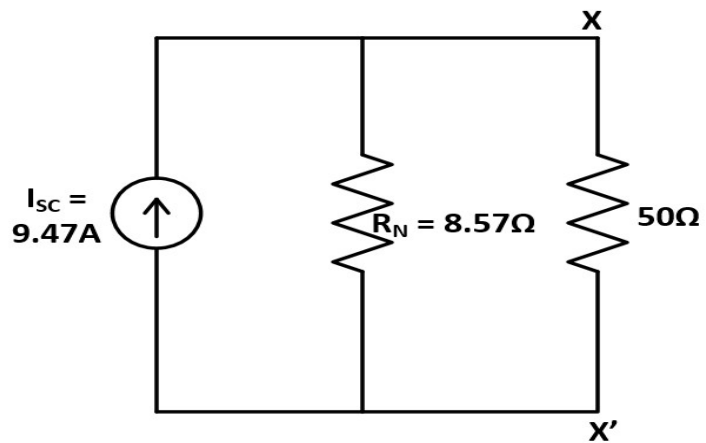


Fig. 1\_8

$$\text{Voltage across } xx' = I_{sc} \frac{8.57}{(8.57+50)} \times 50 = \mathbf{69.27\ V}.$$

**Sol-3.** Two supernodes are to be established as shown in Fig.2. From inspection it is clear that,

$$V_1 = -12V \quad (1)$$

At node 2

$$\frac{V_2 - V_1}{0.5} + \frac{V_2 - V_3}{2} = 14 \quad (2)$$

At 3-4 supernode

$$0.5V_x = \frac{V_3 - V_2}{2} + \frac{V_4}{1} + \frac{V_4 - V_1}{2.5} \quad (3)$$

The two voltage relations are

$$V_3 - V_4 = 0.2V_y \quad (4)$$

and

$$0.2V_y = 0.2(V_4 - V_1) \quad (5)$$

Finally for the dependent current source

$$0.5V_x = 0.5(V_2 - V_1) \quad (6)$$

Substituting  $0.5V_x$  from eq.6 into eq.3, eliminates  $V_x$  and substituting  $0.2V_y$  from eq.5 into eq.4 eliminates  $V_y$ .

Hence, the set of four equations is

$$-2V_1 + 2.5V_2 - 0.5V_3 = 14$$

$$0.1V_1 - V_2 + 0.5V_3 + 1.4V_4 = 0$$

$$V_1 = -12$$

$$0.2V_1 + V_3 - 1.2V_4 = 0$$

Solving above equations

$$V_1 = -12V$$

$$V_2 = -4V$$

$$V_3 = 0V$$

$$V_4 = -2V$$

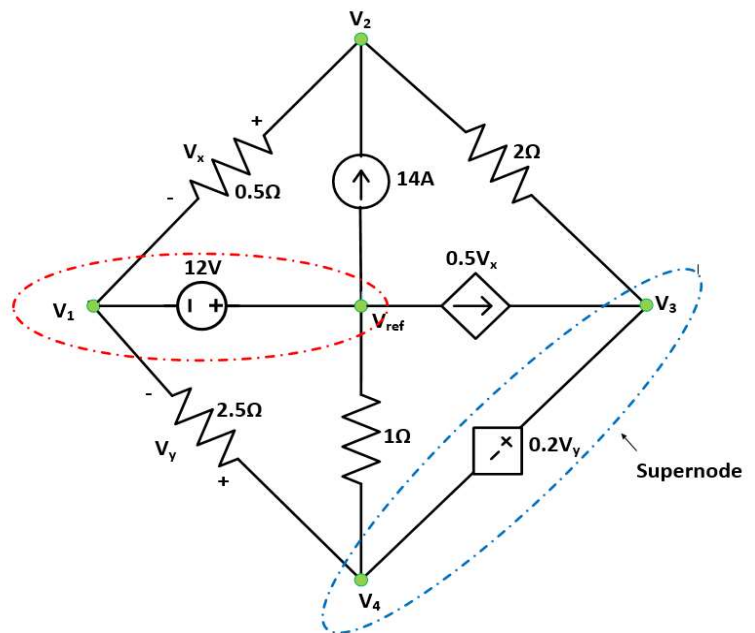


Fig.2 : Figure for Solution 2

**Sol-4.** We first need to replace the circuit by its Thevenin equivalent at terminals **a** and **b**. The Thevenin resistance is found using the circuit shown in Fig.3.

Notice the  $3\text{k}\Omega$  and  $1\text{k}\Omega$  resistors are in parallel; so are  $400\Omega$  and  $600\Omega$  resistors. The two parallel combinations form a series combination with respect to terminals **a** and **b**. Hence,

$$R_{th} = 3000 || 1000 + 400 || 600 = 990\Omega$$

To find the Thevenin voltage, we consider the circuit in Fig.4. Using the voltage division principle gives

$$V_a = \frac{1000}{1000 + 3000} \times 220 = 55V$$

$$V_b = \frac{600}{600 + 400} \times 220 = 132V$$

Applying KVL around loop **ab** gives

$$-V_a + V_{th} + V_b = 0$$

$$\Rightarrow V_{th} = V_a - V_b = 55 - 132 = -77V$$

Having determined the Thevenin equivalent, we find the current through the galvanometer using Fig.5.

$$I_G = \frac{V_{Th}}{R_{Th} + R_m} = \frac{-77}{990 + 40} = -74.76\text{mA}$$

The negative sign indicates that the current flows in the direction opposite to the one assumed, that is, from terminal **b** to terminal **a**.

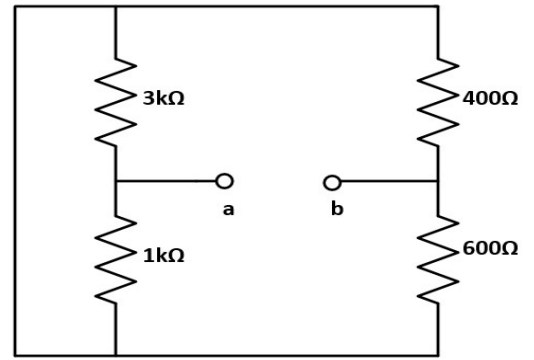


Fig.3

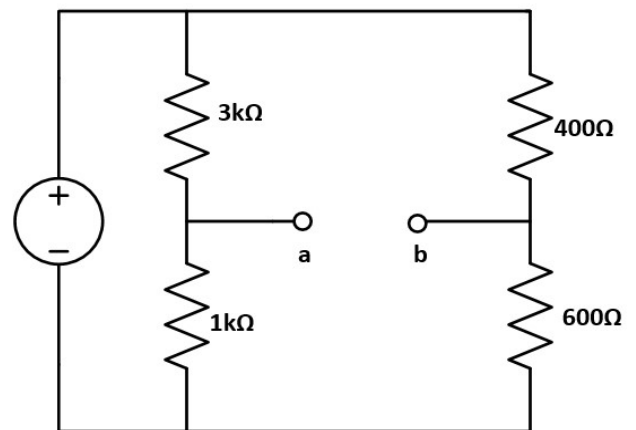


Fig.4

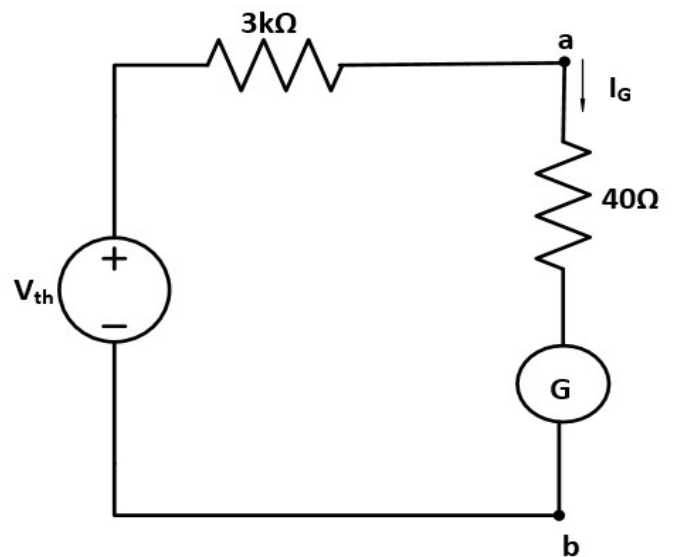


Fig.5