

**EE 101: Electrical Sciences, Tutorial - 3**  
**DEPARTMENT OF ELECTRONICS & ELECTRICAL ENGINEERING**  
**INDIAN INSTITUTE OF TECHNOLOGY GUWAHATI**

**Name :** \_\_\_\_\_ **Roll No. :** \_\_\_\_\_ **Tutorial Group :** \_\_\_\_\_  
[Q1 is for pre-tutorial. Solve it in the space provided and submit at beginning of tutorial]

**Q-1**      $F(A, B, C, D) = \sum(6, 9, 10, 11, 14, 15) + d(2, 7, 8, 13).$

Using K-map solve for (a) minimal SOP form (b) minimal POS form.

**Q-2** Find the voltage across terminal pair  $xx'$  for the network shown in Fig.1 using:

- (a) Thevenin Equivalent circuit
- (b) Norton Equivalent circuit

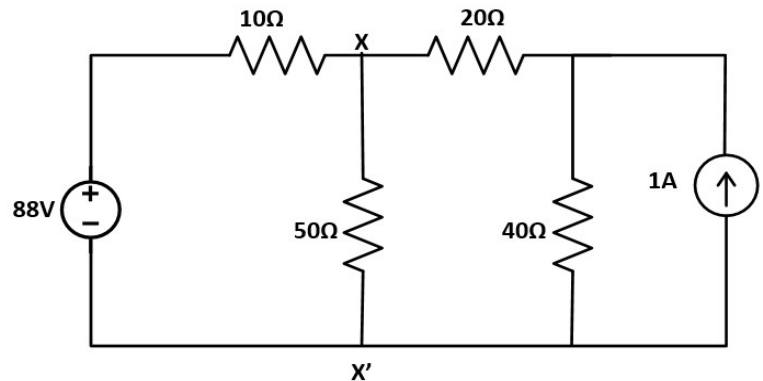


Fig.1

**Q-3** Determine the node voltages for the network shown in Fig.2.

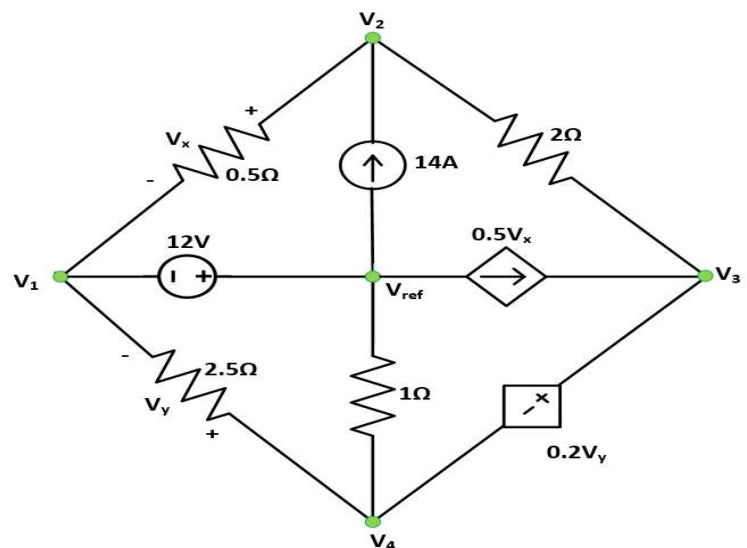


Fig.2

**Q-4** The circuit shown in Fig.3 represents an unbalanced bridge. If the galvanometer has a resistance of 40 Ohms, find the current through the galvanometer. (Hint: Use Thevenin's equivalent circuit)

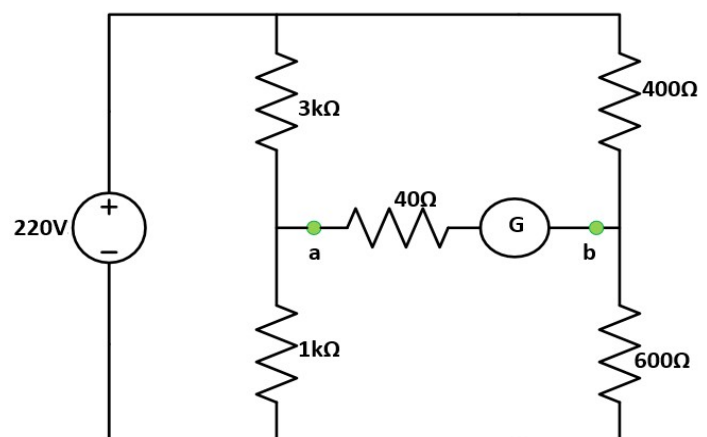


Fig.3